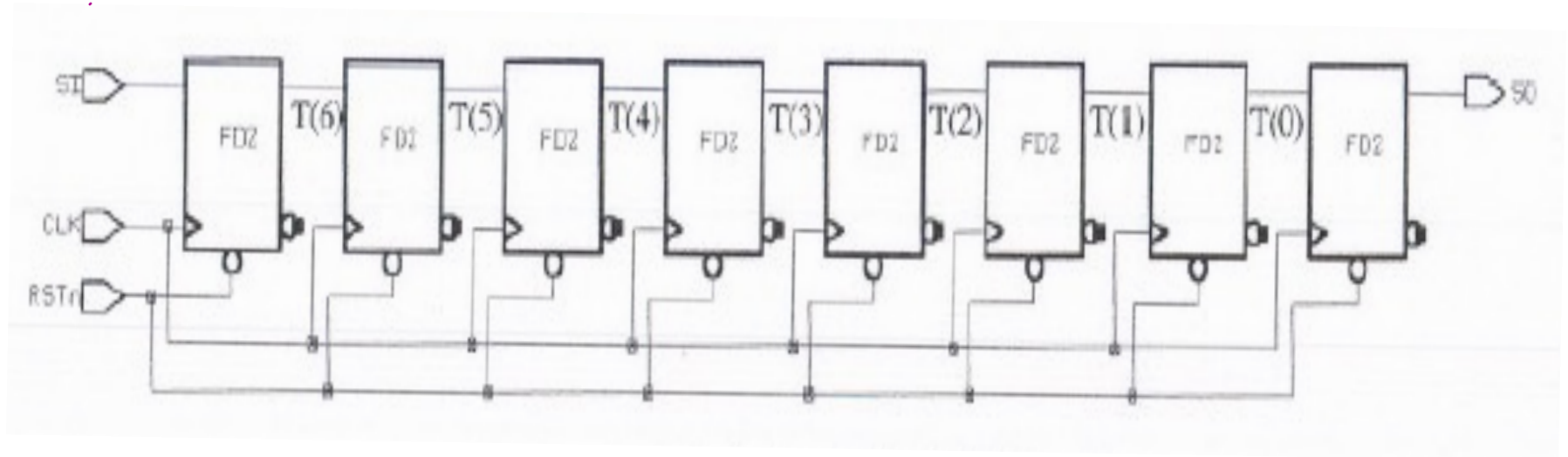



Component Instantiation using GENERATE

Component Instantiation using GENERATE

- 8-b shifter register***
- 24-b shifter register with 3 8-b shifter register***
- GENERATE statement***
- GENERATE examples***

 Component Instantiation: 8-b shifter register





```

entity DFF is
    port (
        RSTn, CLK, D : in bit;
        Q             : out bit);
end DFF;
architecture RTL of DFF is
begin
    process (RSTn, CLK)
    begin
        if (RSTn = '0') then
            Q <= '0';
        elsif (CLK'event and CLK = '1')
        then
            Q <= D;
        end if;
    end process;
end RTL;

```

```

-----
entity SHIFT is
    port (
        RSTn, CLK, SI : in bit;
        SO             : out bit);
end SHIFT;

```

```

architecture RTL1 of SHIFT is
    component DFF
    port (
        RSTn, CLK, D : in bit;
        Q             : out bit);
    end component;
    signal T : bit_vector(6 downto 0);
begin
    bit7 : DFF
        port map (RSTn => RSTn, CLK => CLK, D => SI,
        Q => T(6));
    bit6 : DFF
        port map (RSTn, CLK, T(6), T(5));
    bit5 : DFF
        port map (RSTn, CLK, T(5), T(4));
    bit4 : DFF
        port map (CLK => CLK, RSTn => RSTn, D =>
        T(4), Q => T(3));
    bit3 : DFF
        port map (RSTn, CLK, T(3), T(2));
    bit2 : DFF
        port map (RSTn, CLK, T(2), T(1));
    bit1 : DFF
        port map (RSTn, CLK, T(1), T(0));
    bit0 : DFF
        port map (RSTn, CLK, T(0), SO);
end RTL1;


```

Component Instantiation: 24-b shifter Register

```

entity SHIFT24 is
  port (
    RSTn, CLK, SI : in bit
    SO             : out bit
  )
end SHIFT24;
architecture RTL5 of SHIFT24
  component SHIFT
  port (
    RSTn, CLK, SI : in bit;
    SO           : out bit
  )
end component;
  signal T1, T2 : bit;
begin
    stage2 : SHIFT
      port map (RSTn => RSTn, CLK => CLK, SI => SI, SO => T1);
    stage1 : SHIFT
      port map (RSTn => RSTn, CLK => CLK, SI => T1, SO => T2);
    stage0 : SHIFT
      port map (RSTn => RSTn, CLK => CLK, SI => T2, SO => SO);
  end RTL5;

```

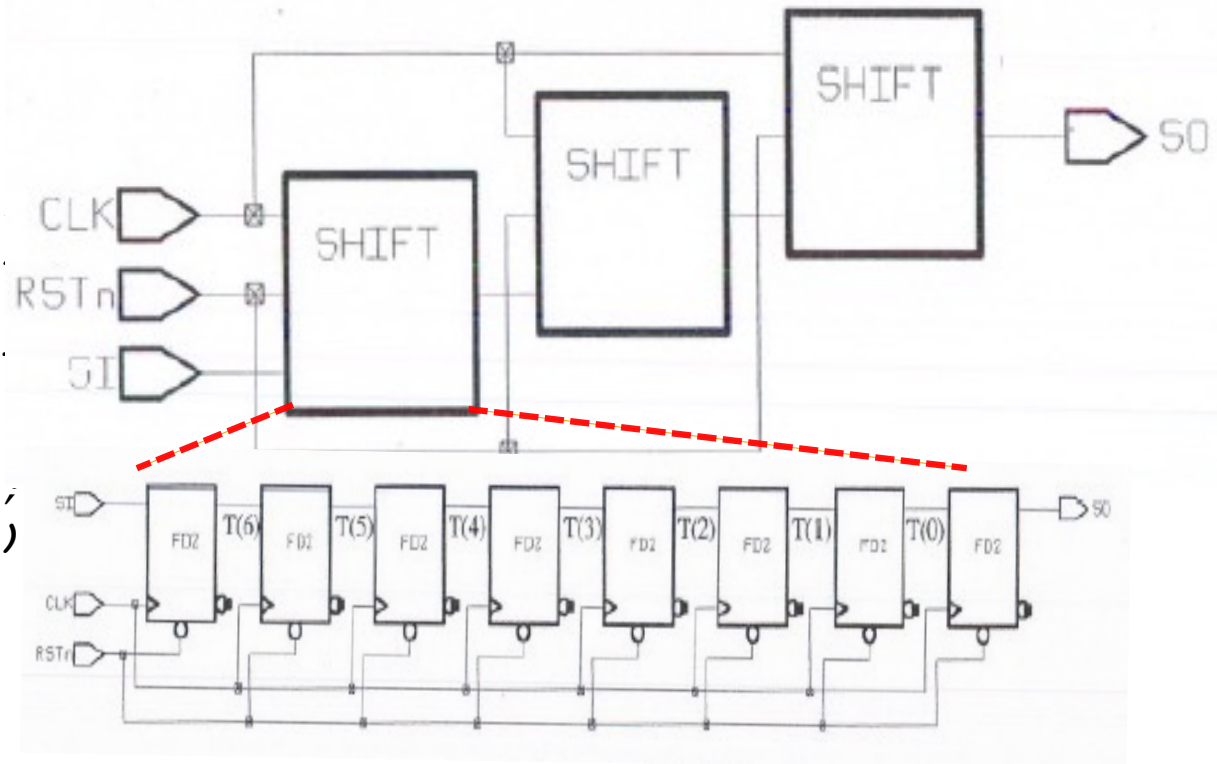

Generate Statement

generate statement ::=


**generate_label: for generate_parameter_spec generate | if
condition generate**

concurrent statements

end generate [generate_label];

optional

 - ☐ **Generate statement is a concurrent statement.**
- ☐ **If statement and for loop statements are sequential statements.**
- ☐ **The if condition generate statement does not have else, elsif clause.**
- ☐ **A label is required for a generate statement.**



```

component DFF
port ( RSTn, CLK, D : in bit;
      Q : out bit);
end component;

```

```

signal T : bit_vector(6 downto 0);

```

```

begin

```

```

g0 : for i in 7 downto 0 generate

```

```

g1 : if (i = 7) generate

```

```

bit7 : DFF

```

```

port map (RSTn => RSTn, CLK => CLK, D => SI, Q => T(6));

```

```

end generate;

```

```

g2 : if (i > 0) and (i < 7) generate

```

```

bitm : DFF

```

```

port map (RSTn, CLK, T(i), T(i-1));

```

```

end generate;

```

```

g3 : if (i = 0) generate

```

```

bit0 : DFF

```

```

port map (RSTn, CLK, T(0), SO);

```

```

end generate;

```

```

end generate;

```

```


end RTL2;

```

use for-loop to
instantiate DFF 8 times

Top generate label

3 sub-generate

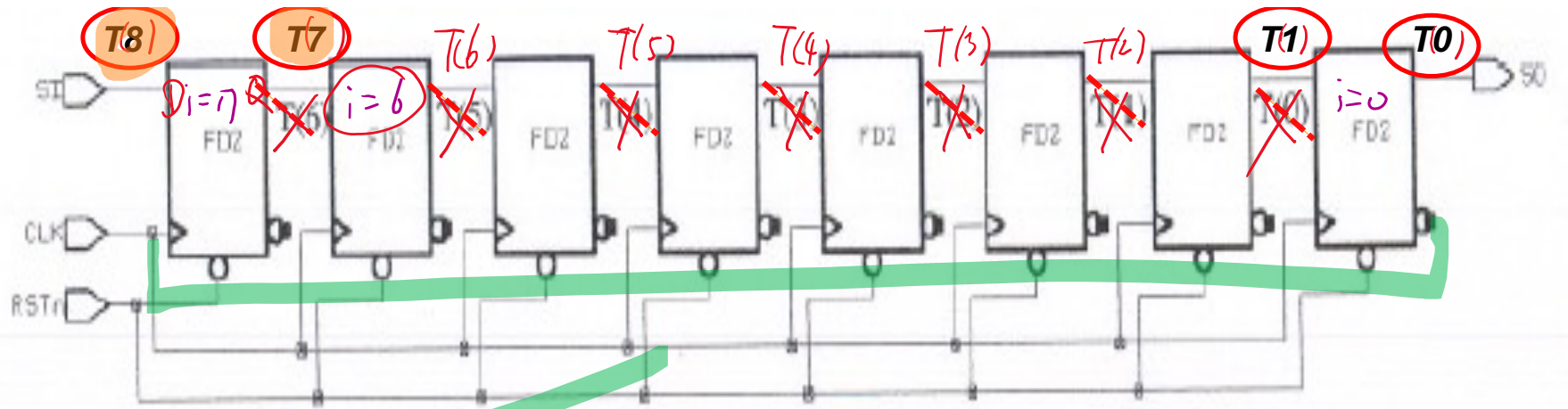

architecture *RTL3* of *SHIFT* is
component *DFF*

port (
 RSTn, *CLK*, *D* : in bit;
 Q : out bit);

end component;

signal *T* : bit_vector(8 downto 0);

begin

T(8) <= *SI*;

SO <= *T*(0);

g0 : for *i* in 7 downto 0 generate

allbit : *DFF* *i*=7

port map (*RSTn* => *RSTn*, *CLK* => *CLK*, *D* => *T*(*i*+1), *Q* => *T*(*i*));

end generate;

end *RTL3*;

**New signal declaration
=> One generate statement**


```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
ENTITY byte_adder IS
PORT(  A,B : IN STD_LOGIC(31 DOWNT0 0);
      CIN : IN STD_LOGIC;
      S : OUT STD_LOGIC(31 DOWNT0 0);
      CO : OUT STD_LOGIC );
END ENTITY;

```

```

ARCHITECTURE arch_byt OF byte_adder IS

```

```

COMPONENT fa IS
PORT(  a,b,cin : IN STD_LOGIC;
      sum,cout : OUT STD_LOGIC);
END COMPONENT;

```

```

COMPONENT xor2 IS
PORT(  a,b : IN STD_LOGIC;
      c : OUT STD_LOGIC);
END COMPONENT;

```

```


SIGNAL SIG,CAR : STD_LOGIC(31 DOWNT0 0);

```


```

BEGIN
  CAR(0) <= CIN;
  GK: FOR k IN 31 DOWNT0 0 GENERATE
    X1 : xor2 PORT MAP ( CIN, B(k), SIG(k));
    F1 : fa PORT MAP(A(k), SIG(k), CAR(k), S(k), CAR(k+1))
  END GENERATE GK;
  COUT <= CAR(32);
END ARCHITECTURE arch_byt;

```

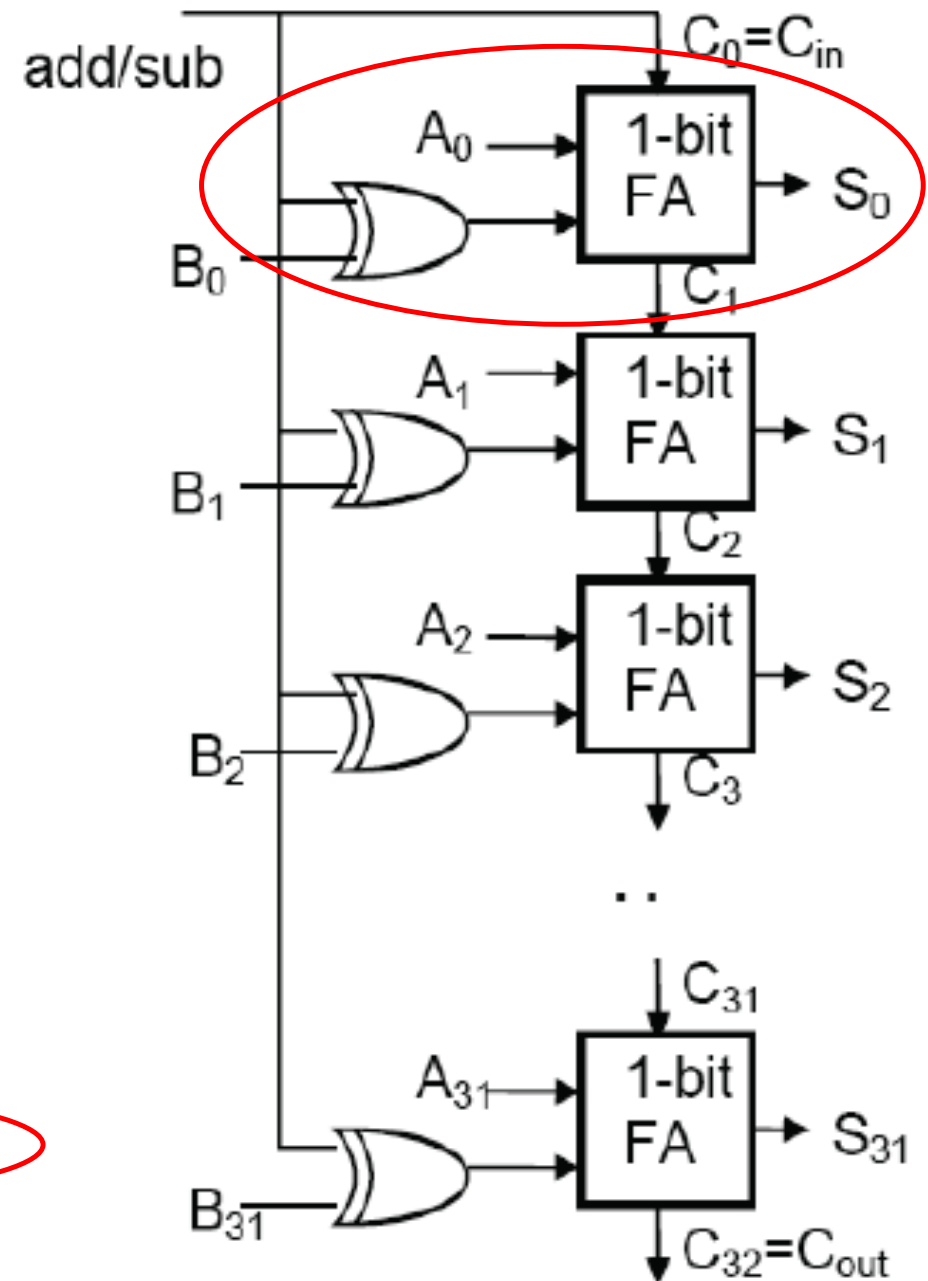

Example:

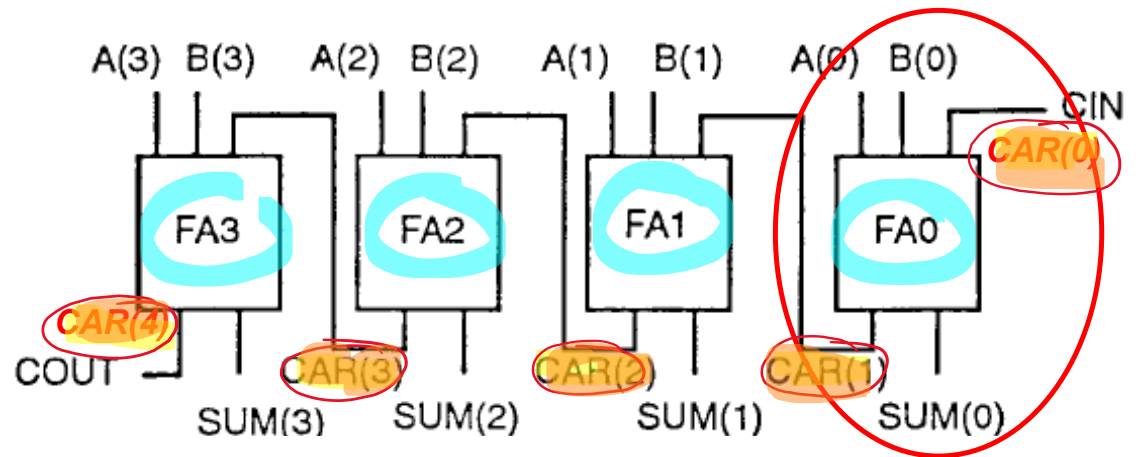

```
entity FULL_ADD4 is
port (A, B: in BIT_VECTOR(3 downto 0); CIN: in BIT;
SUM: out BIT_VECTOR(3 downto 0); COUT: out BIT);
end FULL_ADD4;
```

```
architecture FOR_GENERATE of FULL_ADD4 is
component FULL_ADDER
port (A, B, C: in BIT; COUT, SUM: out BIT);
end component;
```

```
signal CAR: BIT_VECTOR(4 downto 0);
```

```
begin
```

```
  CAR(0) <= CIN;
```

```
  GK: for K in 3 downto 0 generate
```


```
    FA: FULL_ADDER port map (CAR(K), A(K), B(K), CAR(K+1), SUM(K));
```

```
  end generate GK;
```

```
  COUT <= CAR(4);
```

```
end FOR_GENERATE;
```

Example:

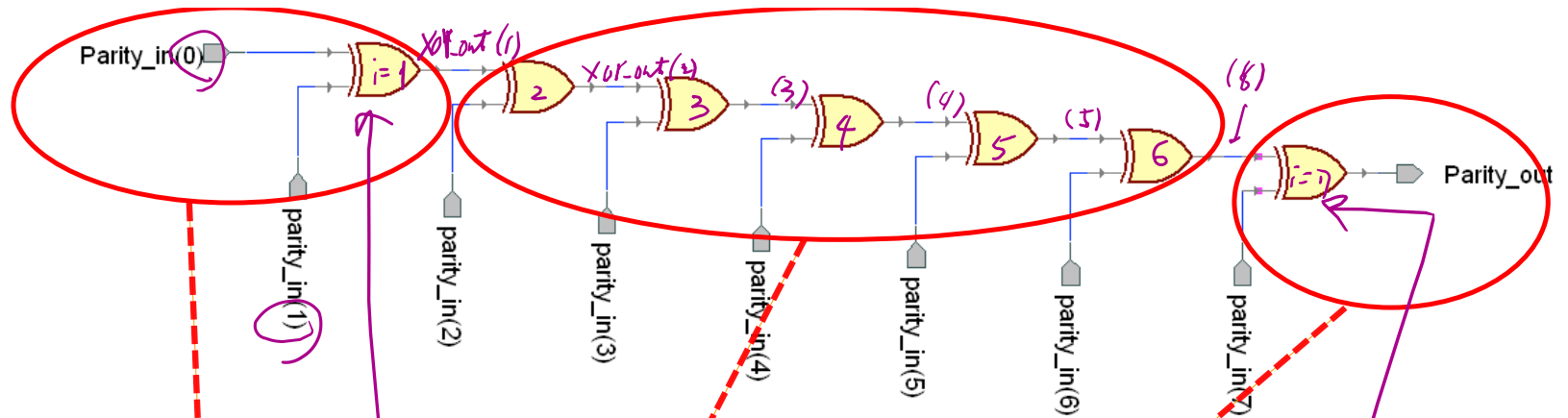

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (6 DOWNTO 1);

BEGIN

G2: FOR i IN 1 TO 7 GENERATE

left_xor: IF i=1 GENERATE

xor_out(i) <= parity_in(i-1) XOR parity_in(i);

END GENERATE;

middle_xor: IF (i>1) AND (i<7) GENERATE

xor_out(i) <= xor_out(i-1) XOR parity_in(i);

END GENERATE;

right_xor: IF i=7 GENERATE

parity_out <= xor_out(i-1) XOR parity_in(i);

END GENERATE;

END GENERATE;


END parity_dataflow;

top

Sub-generator

Boolean

Example:

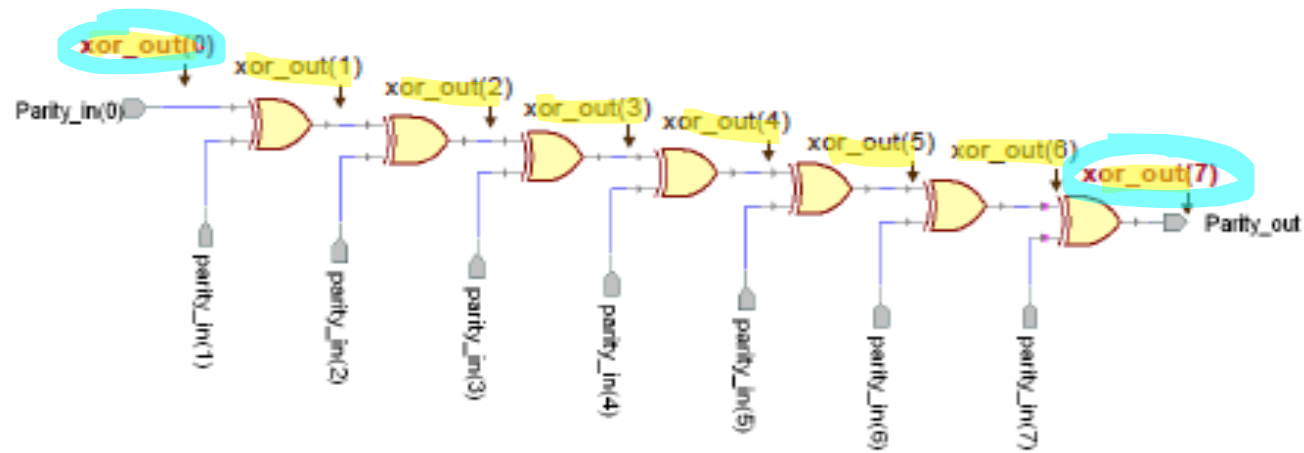

ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (7 DOWNTO 0);

BEGIN

xor_out(0) <= parity_in(0);

G2: FOR i IN 1 TO 7 GENERATE
xor_out(i) <= xor_out(i-1) XOR parity_in(i);
END GENERATE G2;

parity_out <= xor_out(7);

END parity_dataflow;

**New signal declaration
=> One generate statement**

one generate