

1. [30 pts] Below is a behavioral VHDL code.

```
entity priority_4in is
  port ( inputs : in std_logic_vector(3 downto 0);
        result : out std_logic_vector(1 downto 0);
        valid  : out std_logic; );
end priority_4in;
```

```
architecture if_statement of priority_4in is
begin
  process(inputs)
  begin
    if (inputs(3) = '1') then
      result <= "11";
      valid  <= '1';
    elsif (inputs(2) = '1') then
      result <= "10";
      valid  <= '1';
    elsif (inputs(1) = '1') then
      result <= "01";
      valid  <= '1';
    elsif (inputs(0) = '1') then
      result <= "00";
      valid  <= '1';
    else
      result <= "00";
      valid  <= '0';
    end if;
  end process;
end if_statement;
```

- a) [15 pts] Construct the truth table and derive the optimized *Boolean expressions for the outputs*.

[blank]

b) [15 pt] Use **case** statement to complete the VHDL code.

entity priority\_4in is

port (

inputs : in std\_logic\_vector(3 downto 0);

result : out std\_logic\_vector(1 downto 0);

valid : out std\_logic;

);

end priority\_4in;

architecture case\_statement of priority\_4in is

begin

process(inputs)

begin

--- use **case** statement

end process;

end case\_statement;

2. [30 pts] A function takes a binary vector of any size as input and returns an integer representing the **maximum consecutive 1's** in the input vector. It iterates through each element of the input vector, and finally, it returns **max\_count**, which represents the **maximum consecutive 1's** in the input vector. The following VHDL defines an entity named **MaxConsecutiveOnesEntity** with an 8-bit input vector (**input\_vector**) and an output representing **the maximum consecutive 1's (max\_count\_output)**. In the architecture, a process is used to call the **max\_consecutive\_ones** function with the **input\_vector** and assign the result to **max\_count\_output**.  
For example: If the input\_vector is “00**1111**00” then the output, max\_count\_output = 4. If the input DATA is “**111**00010” or “10010**111**” then the output, max\_count\_output = 3.

entity **MaxConsecutiveOnesEntity** is

```
port (  
    input_vector : in std_logic_vector(7 downto 0); -- Example: 8-bit input vector  
    max_count_output : out integer -- Output representing max consecutive 1's  
);  
end entity MaxConsecutiveOnesEntity;
```

architecture Behavioral of MaxConsecutiveOnesEntity is

```
    function max_consecutive_ones (in_vector : std_logic_vector) return integer is
```

```
        end function max_consecutive_ones;
```

```
begin
```


```
    process(input_vector)
```

```
        end process;
```

```
end architecture Behavioral;
```


3. [30 pts] Below is a Booth action and architecture stage for Booth multiplication.

$y_i$	$y_{i-1}$	$y_{i-2}$	increment
0	0	0	0
0	0	1	x
0	1	0	x
0	1	1	2x
1	0	0	-2x
1	0	1	-x
1	1	0	-x
1	1	1	0

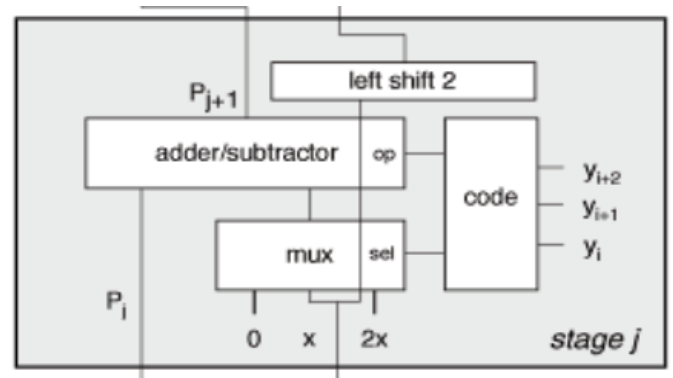

- a) [15 pts] Use 7-bit 2's complement number system, Booth encoding and algorithm to explain the Booth multiplication of  $x = 1001101$  and  $y = 1011011$ . **Note: Show your bit operation step-by-step and find ALL partial products** (in 2's complement).

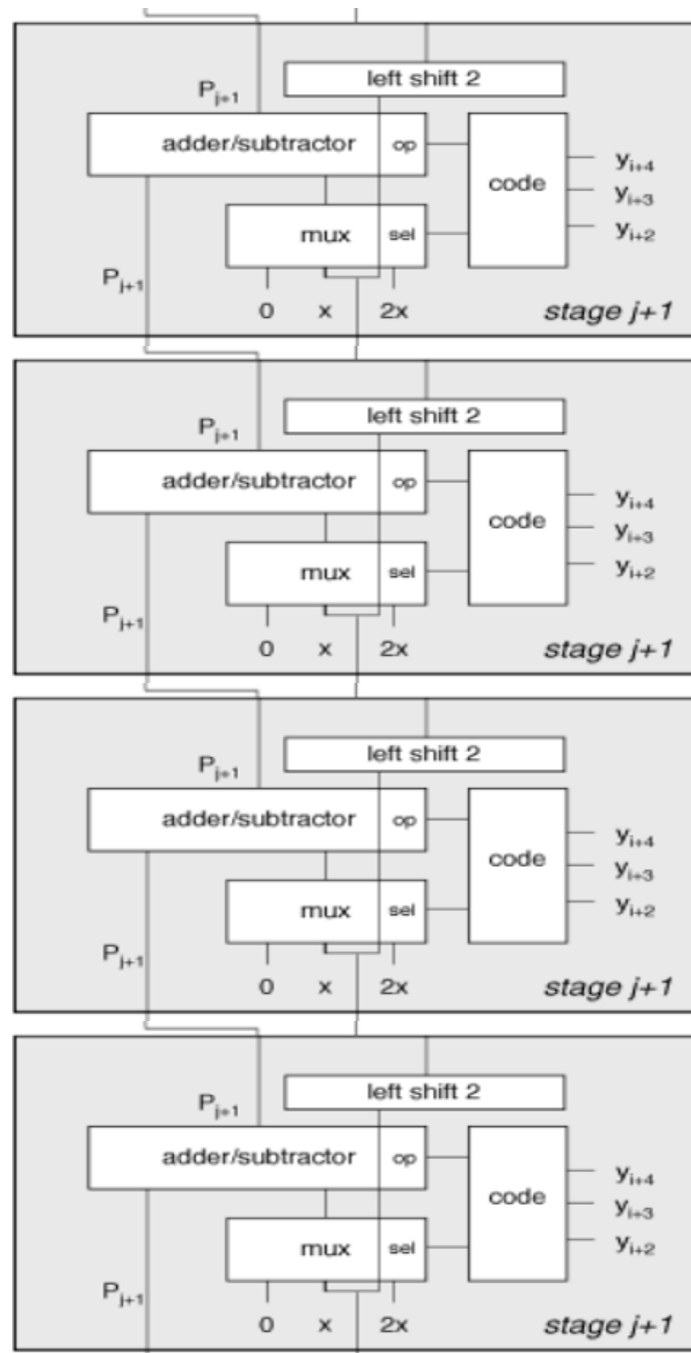- b) [15 pts] Draw Booth multiplier architecture to implement the Booth multiplication of  $x = 1001101$  and  $y = 1011011$ . Show how data (in 2's complement) is propagated and your **bit operation** through every architecture stage. Include  $(y_i y_{i+1} y_{i+2})$  bits, your “mux” output bits, “adder/subtractor” output bits, and “left shift 2” output bits in your architecture.



4. [40 pts]
- A) [20 pts] Consider two fixed-number numbers A and B where,  $A = -3.75$  and  $B = 2.75$ . **Use 2's complement number, I3.Q2 format, for both A and B.** Calculate the following calculation results.
- a) [4 pts] What is your **I3.Q2 format** result for A?
- b) [4 pts] What is your **I3.Q2 format** result for B?
- c) [4 pts] What is your **I3.Q2 format** result for -B?
- d) [4 pts] Calculate  $A + B$  and find your final **I4.Q2 format** result. Note: show your bit operation.
- e) [4 pts] Calculate  $A - B$  and find your final **I4.Q2 format** result. Note: show your bit operation.

B) [20 pts]

**Note: In the following (h) ~ (k), you must use the exact multiplicand and multiplier in your calculation. Also, you cannot switch both.  $A = -3.75$  and  $B = 2.75$ .**

f) [10 pts] Calculate  $A \times B$  and find your final **I5.Q5 format** result. Note: show your bit operation.

g) [10 pts] Calculate  $A \times (-B)$  and find your final **I5.Q5 format** result. Note: show your bit operation.



5. [40 pts (including Bonus 20 pts)] A **counter** that counts from **0 to 31** in integer has input ports **RSTn**, **CLK**, **EN**, **PL**, and **DATA**. **The output port COUNT receives the value of the counter.** **RSTn** serves as the asynchronous reset, while **CLK** is the clock input signal. The asynchronous reset **RSTn** is prioritized, activated by verifying if **RSTn** is '0', and initializing the counter to 0 before considering the rising edge trigger of the clock. If **CLK** is **rising edge-triggered**, the synchronous behavior of either the **parallel load** or **count model** of the counter is modeled.

Note: 1) Parallel load (PL) takes precedence over the count enable (EN). PL = '1' is checked first, and EN = '1' is only checked when PL = '1' is not TRUE.

2) When PL is '1', the counter performs the **parallel load**, loaded with the **DATA** value.

3) When PL = '0' and EN = '1', the counter starts the count mode. The counter is triggered to increment its count on the rising edge of the clock signal (**CLK**). **It's important to note that after the counter reaches the value (31), it resets to the initial value (0).**

4) When PL = '0' and EN = '0', the counter holds its previous value.

5) COUNT is declared as an output port; however, VHDL does not allow the output port signal of COUNT to be read. Therefore, a temporary signal **COUNT\_VALUE** is declared and used in the process. Finally, COUNT\_VALUE is assigned to the output port COUNT outside the process.

entity FiveBitCounter is

port (

RSTn : in std\_logic;

CLK : in std\_logic;

EN : in std\_logic;

PL : in std\_logic;

DATA : in integer;

COUNT : out integer;

);

end entity FiveBitCounter;

architecture Behavioral of FiveBitCounter is

**variable COUNT\_VALUE : integer;**

begin


process(CLK, RSTn)

end architecture Behavioral;

[blank]

6. [50 pts]

 a) [20 pts] A D flip-flop with an **asynchronous reset** input and an **enable** input is given below. Complete the following entity and architecture pair of the D flip-flop. The DFF has an **asynchronous reset** “Reset”, i.e., the output  $Q = 0$  when  $\text{Reset} = 1$ . The **Reset** has a higher priority than the **clock**. And, the **clock** has a higher priority than the **enable ‘E’**. The **enable ‘E’** controls the multiplexer input selection, i.e.,  $E = 0$  selects the flip-flop’s output,  $Q$ ;  $E = 1$  selects  $R \text{ XOR } Q$ ; The DFF loads new data only when  $\text{Reset} = 0$  and the clock in **rising edge trigger**.



entity **rege** is

port (R, Reset, Clock, E: in bit;

Q: out bit);

end entity rege;

ARCHITECTURE Behavior OF rege IS

BEGIN


PROCESS (Reset, Clock)

BEGIN

END PROCESS ;

END Behavior ;

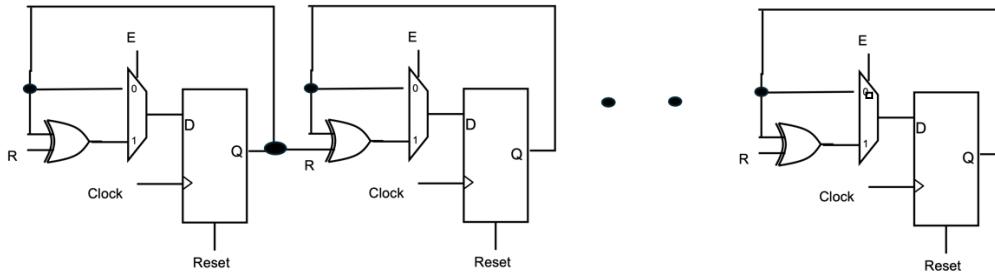b) [15 pts] Use "generate" statements to write an entity and architecture pair of VHDL description for a 16-bit wide using 1-bit **rege** as described in (a). Complete the following 16-bit wide using **3 GENERATE** statements.



entity **rege\_16** is  
 port (D, Reset, E, Clock: in bit; Y: out bit);  
end entity rege\_16;


architecture reg16 of **rege\_16** is  
 -- component declaration  
 component **rege**  
 port (R, Reset, Clock, E: in bit;  
 Q: out bit);  
end component rege;

b.1) [5 pts] --- **signal declaration** (Note: Write your signals on the above 16-bit wide shift registers logic.)

b.2) [10 pts] --- Use **3 GENERATE** statements  
 --- Use **port map by POSITION**.

begin

end architecture;

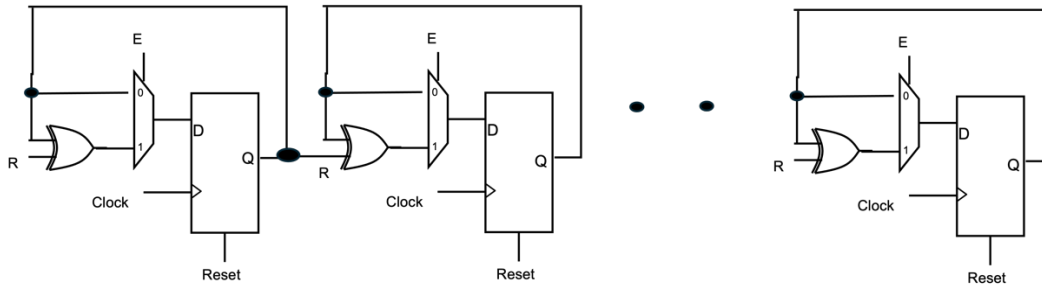

c) [15 pts] Complete the 16-bit wide shift registers using only one GENERATE statement.

```
entity rege_16 is
  port (D, Reset, Clock, E: in bit;
        Q: out bit);
end entity rege_16;
```

architecture reg16 of rege\_16 is

```
-- component declaration
component rege
  port (R, Reset, Clock, E: in bit;
        Q: out bit);
end component rege;
```

c.1) [5 pts] --- signal declaration (Note: Write your signals on the above 16-bit wide shift registers logic.)

c.2) [10 pts] --- Use one GENERATE statement  
 --- Use port map by POSITION.

```
begin
```

```
end architecture;
```