

15 - Voltage Regulators


CEG 4330/6330 - Microprocessor-Based Embedded Systems
Max Gilson

Regulating Voltage

- All microcontrollers and microprocessors require power to run
- The power is delivered by one or more voltage supplies
- These voltage supplies need to run at a specific voltage the microcontroller or microprocessor has been designed to use
- Thus, we will need some form of a regulated voltage supply


Regulating Voltage (cont.)

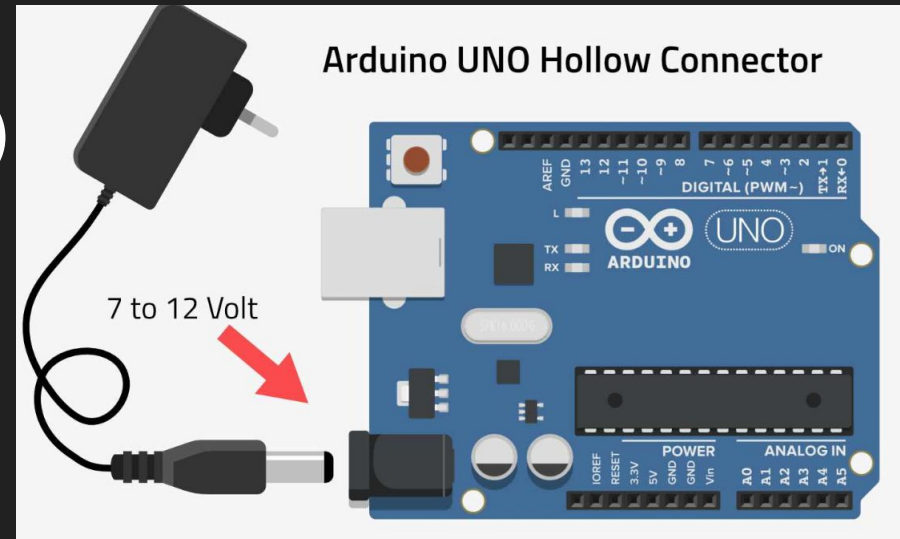- Voltage regulation is typically handled on the circuit board for the embedded system itself
- This makes connecting the embedded system to a main power source much simpler
 - Example: The Arduino's microcontroller requires 5V
 - You can power the Arduino board with 7V to 12V because it gets regulated down to 5V



Arduino Uno Voltage Regulator

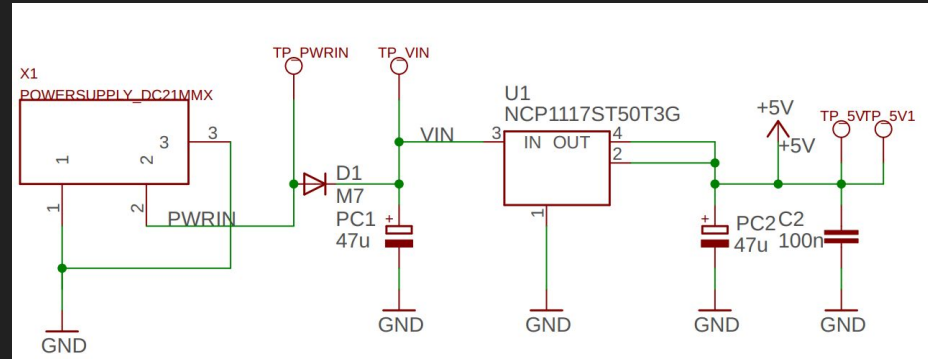- The input voltage for the Arduino board is 7V to 12V recommended (20V max)
- The voltage regulator (U1) takes this input voltage and converts it to 5V




Types of Voltage Regulators

- There are 3 different types of voltage regulators
 - Linear Regulator
 - Low efficiency (wastes power by itself) but simple
 - LDO (Low Dropout Linear Regulator)
 - Medium efficiency also simple
 - Best used with V_{in} is very close to V_{out}
 - Switching Regulator
 - Highest efficiency but more complex



Linear Regulator

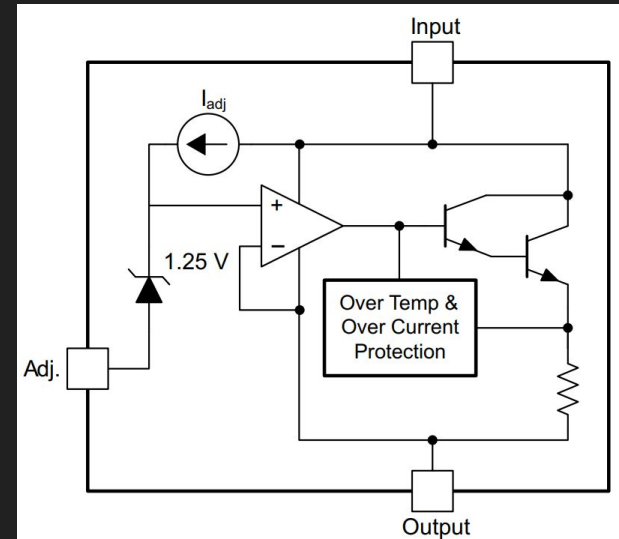- A linear regulator will regulate a wide range of input voltages to some output voltage
- If you do not require efficiency and want a simple design with a high input range, a linear regulator is great
- LM317 is common linear regulator that has an adjustable output voltage
 - Input voltage: 4.25V to 40V
 - Output voltage: 1.25V to 37V




Linear Regulator (cont.)

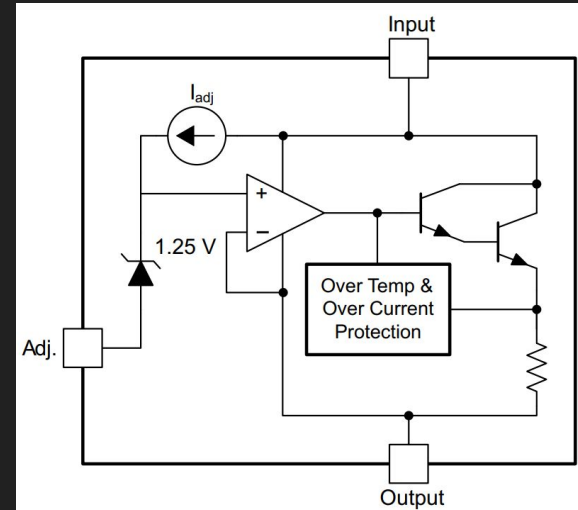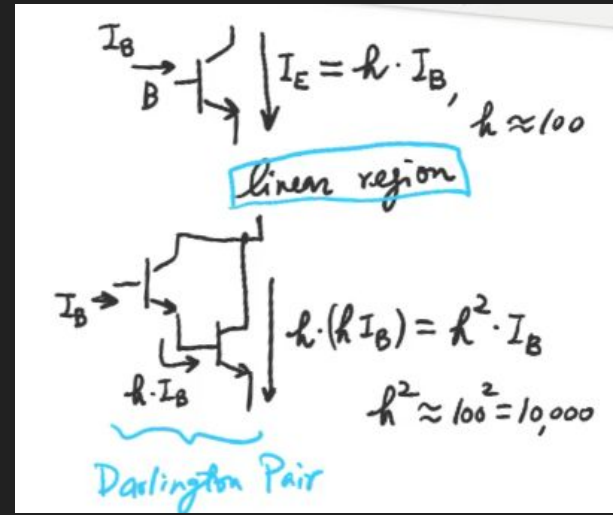- A linear regulator works by exploiting the linear region of transistors in a Darlington Pair
- The linear region of transistor operation is where the output current has a linear relationship to input current
- The Darlington Pair allows for very small amounts of current to control large amounts of current
- The Zener diode provides a fixed reference for the regulator's feedback loop



LM317 Circuit


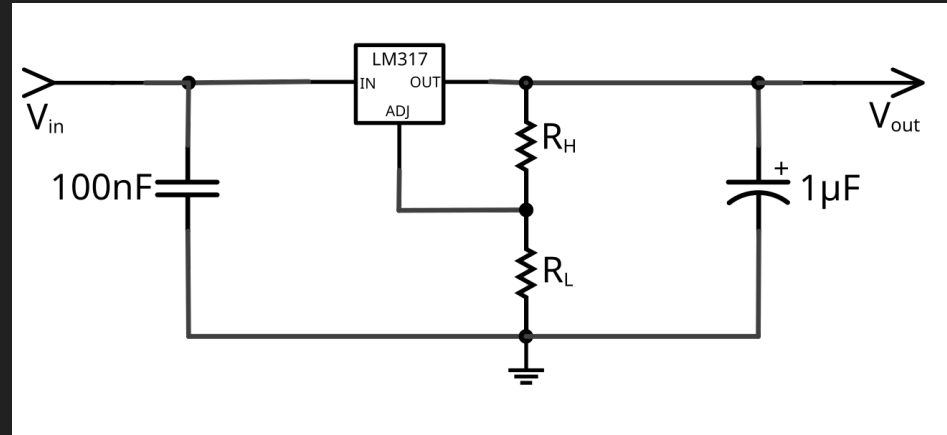
- A circuit for the LM317 is shown
 - Under typical operation V_{ref} is 1.25V
 - To regulate a certain output voltage, you must select R_L and R_H
- Select resistors for $V_{out} = 5V$
 - What is the range for V_{in} ?



$$V_{out} = V_{ref} \left(1 + \frac{R_L}{R_H} \right)$$


Low Dropout Linear Regulator (LDO)

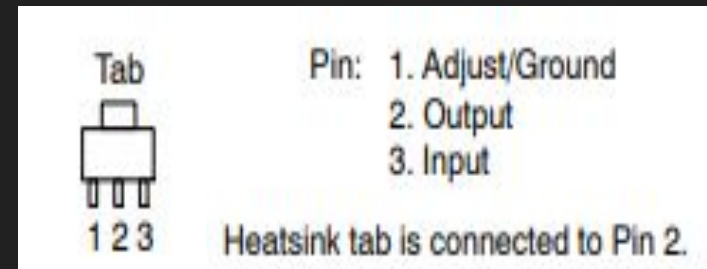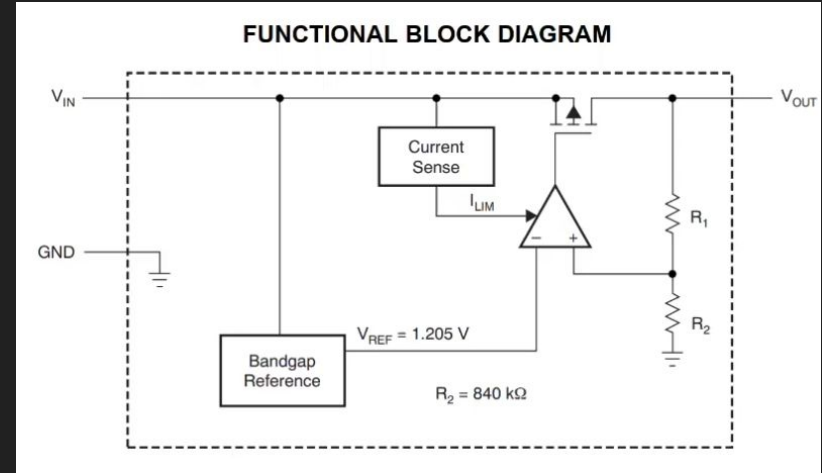- A low dropout linear regulator (LDO) is another form of linear regulator
- It is designed to have very low dropout
 - Dropout is the minimum $V_{in} - V_{out}$ while still achieving desired regulation
- NCP1117 is used by the Arduino board




Low Dropout Linear Regulator (LDO) (cont.)

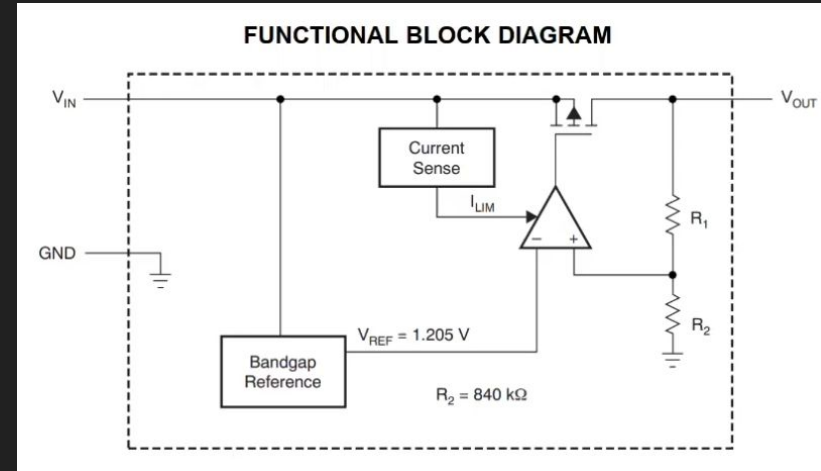- LDOs are more efficient because their voltage drop is lower:
 - $P = I * V$
 - I = load current
 - $V = V_{in} - V_{out}$
 - If $V_{in} = V_{out}$, no power consumption!
 - Efficiency = P_{out} / P_{in}
 - Current is typically equally for input and output
- For this reason, it is much better to select an LDO if V_{in} is very close to V_{out}



NCP1117 Circuit


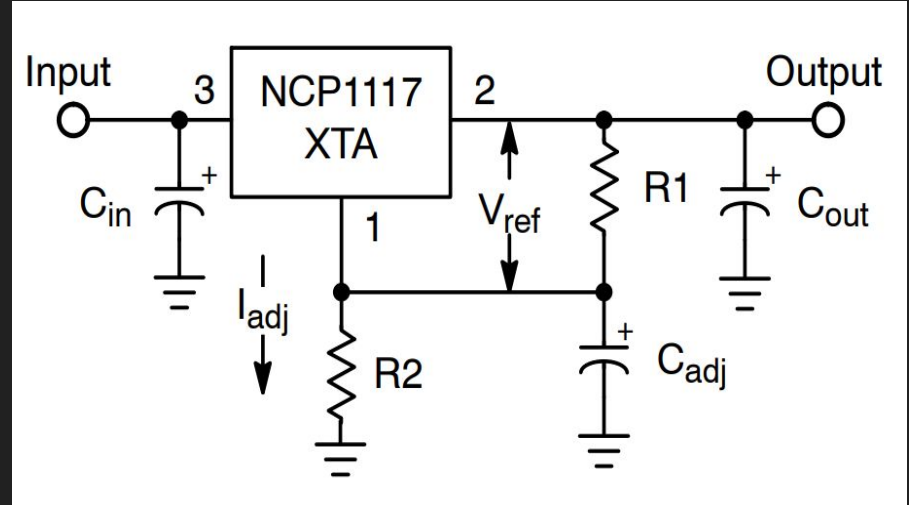
- A circuit for the NCP1117 is shown
 - Under typical operation V_{ref} is 1.25V
 - To regulate a certain output voltage, you must select R1 and R2
- Select resistors for $V_{out} = 5V$
 - What is the range for V_{in} ?



$$V_{out} = V_{ref} \left(1 + \frac{R2}{R1} \right)$$

Switching Regulator

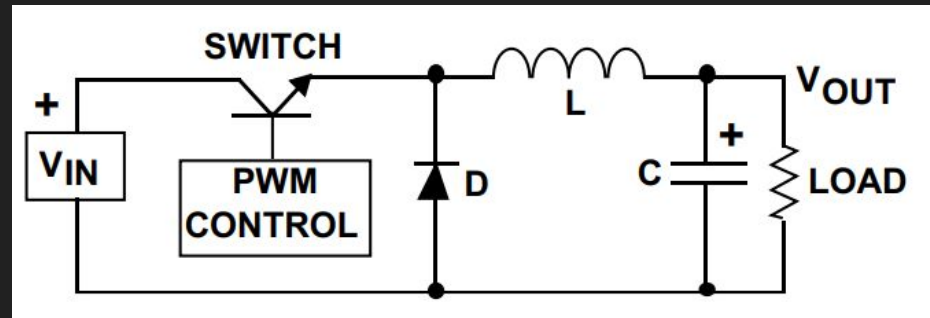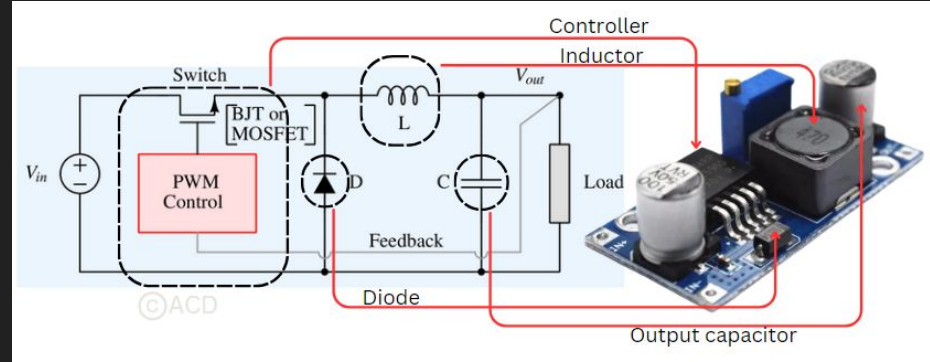- A switching regulator works on the principle of $V = L \, di/dt$ for an inductor
- Very efficient, but creates a lot of noise
- Output voltage can be higher (boost), or lower (buck), or even negative



Buck Regulator

- A buck regulator is a type of switching regulator
 - Also called step down
 - Regulates a $V_{out} < V_{in}$
- Highly efficient because inductor and capacitor consume no power but diode consumes a little power
- $V_L = V_{in} - V_{out}$
- $V_{out} = V_{in} - V_L$
- $V_{out} = V_{in} - L \frac{di}{dt}$
- Try it yourself:

<https://tinyurl.com/236sd32t>


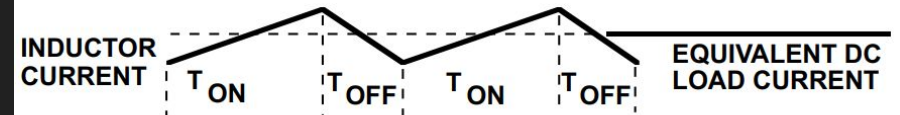
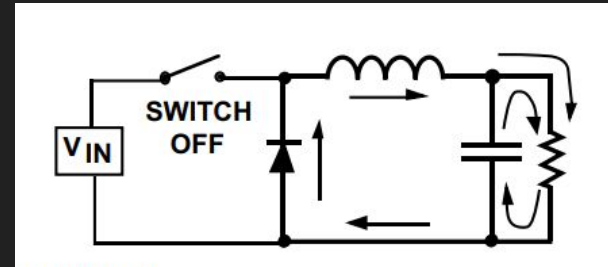
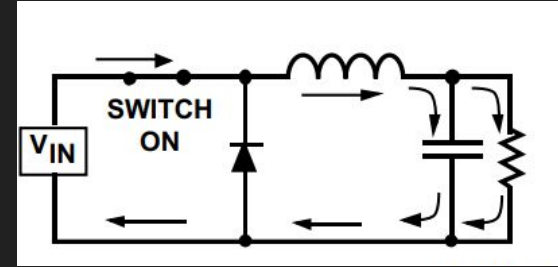


Figure 6. Buck Regulator Inductor Current

Boost Regulator

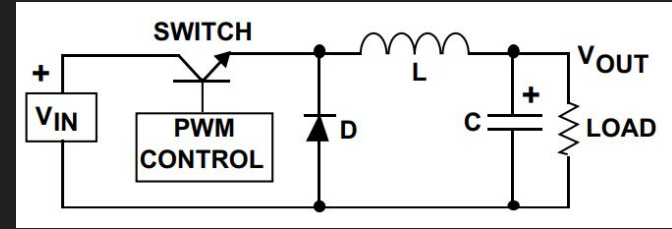- A boost regulator is a type of switching regulator
 - Also called step up
 - Regulates a $V_{out} > V_{in}$
- Also highly efficient
- When the switch opens, the inductor induces a voltage, causing a rise in voltage in V_{out}
- Try for yourself:
<https://tinyurl.com/2279hfbn>

