 


1. Write an entity and architecture pair of VHDL structural description for a structural representation of a circuit sequential\_1 shown below. You need to declare the components (i.e., **DFF1** for D flip-flop, **OR2** for 2-input OR gate, **INV1** for inverter gate, and **MUX2** for 2x1 MUX gate) used in the schematic diagram. Assume these basic components have been compiled. Ensure all signals and ports of **STD\_LOGIC** type and labeled in the schematic diagram match your VHDL code. Use **BY-NAME** method of port mapping.



```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
ENTITY sequential_1 IS
    PORT ( a,b,c,CLK: in STD_LOGIC; out1: out STD_LOGIC;

);
END ENTITY buzzer;
architecture sequential_structure of sequential_1 is

```

```

-- Component and signal declarations
    component INV1
    port (A: in STD_LOGIC; Z: out STD_LOGIC);
    end component;
    component OR2
    port (A,B: in STD_LOGIC; Z: out STD_LOGIC);
    end component
    component MUX2
    port (A,B,Sel: in STD_LOGIC; Z: out STD_LOGIC);
    end component
    component DFF1
    port (D, CLK: in STD_LOGIC; Q: out STD_LOGIC);
    end component
-- declaration of signals used to interconnect gates
    Signal s1, s1, s3: in STD_LOGIC;

```

```

begin

```

```

-- Component instantiations

```

```

end sequential_structural;

```