
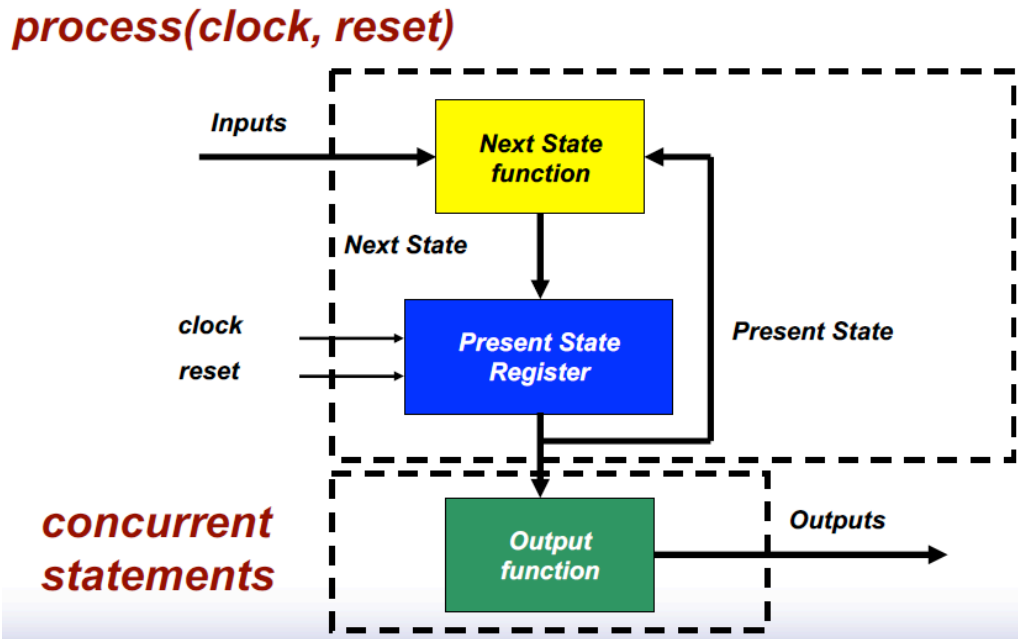


 A. Moore machine 101

Let's construct the **sequence detector for the sequence 101** using Moore state machine. The Output of the State machine depends only on present state. The output of state machine are only updated at the clock edge. *The FSM uses a synchronous reset and clock has a higher priority than reset.*




Moore state machine require four states s_0, s_1, s_2, s_3 to detect the **101** sequence.

VHDL code for Sequence detector (101) using Moore state machine

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity moore is
Port ( clk : in STD_LOGIC;
      din : in STD_LOGIC;
      rst : in STD_LOGIC;
```
 
```
dout : out STD_LOGIC);
end moore;
```



architecture Behavioral of moore is
 type state is (st0, st1, st2, st3);
 signal present_state, next_state : state;
 begin

Next state
 →

```
next_state_decoder : process(present_state, din)
begin
  case (present_state) is
    when st0 =>
      if (din = '1') then
        next_state <= st1;
      else
        next_state <= st0;
      end if;
    when st1 =>
      if (din = '1') then
        next_state <= st1;
      else
        next_state <= st2;
      end if;
    when st2 =>
      if (din = '1') then
        next_state <= st3;
      else
        next_state <= st0;
      end if;
    when st3 =>
      if (din = '1') then
        next_state <= st1;
      else
        next_state <= st2;
      end if;
    when others =>
      next_state <= st0;
  end case;
```

end process;

present state register
synchronous_process: process(clk, rst)

begin

-- Synchronous reset; clock has a higher priority than reset.

if (clk = '1' AND clk'event) then

if (rst = '1') then

present_state <= st0;

else

present_state <= next_state;

end if;

end if;


end process;

output function
dout <= '1' WHEN present_state = st3 ELSE '0';

end Behavioral;


~~next_state <= st0;~~

~~next_state <= present_state;~~

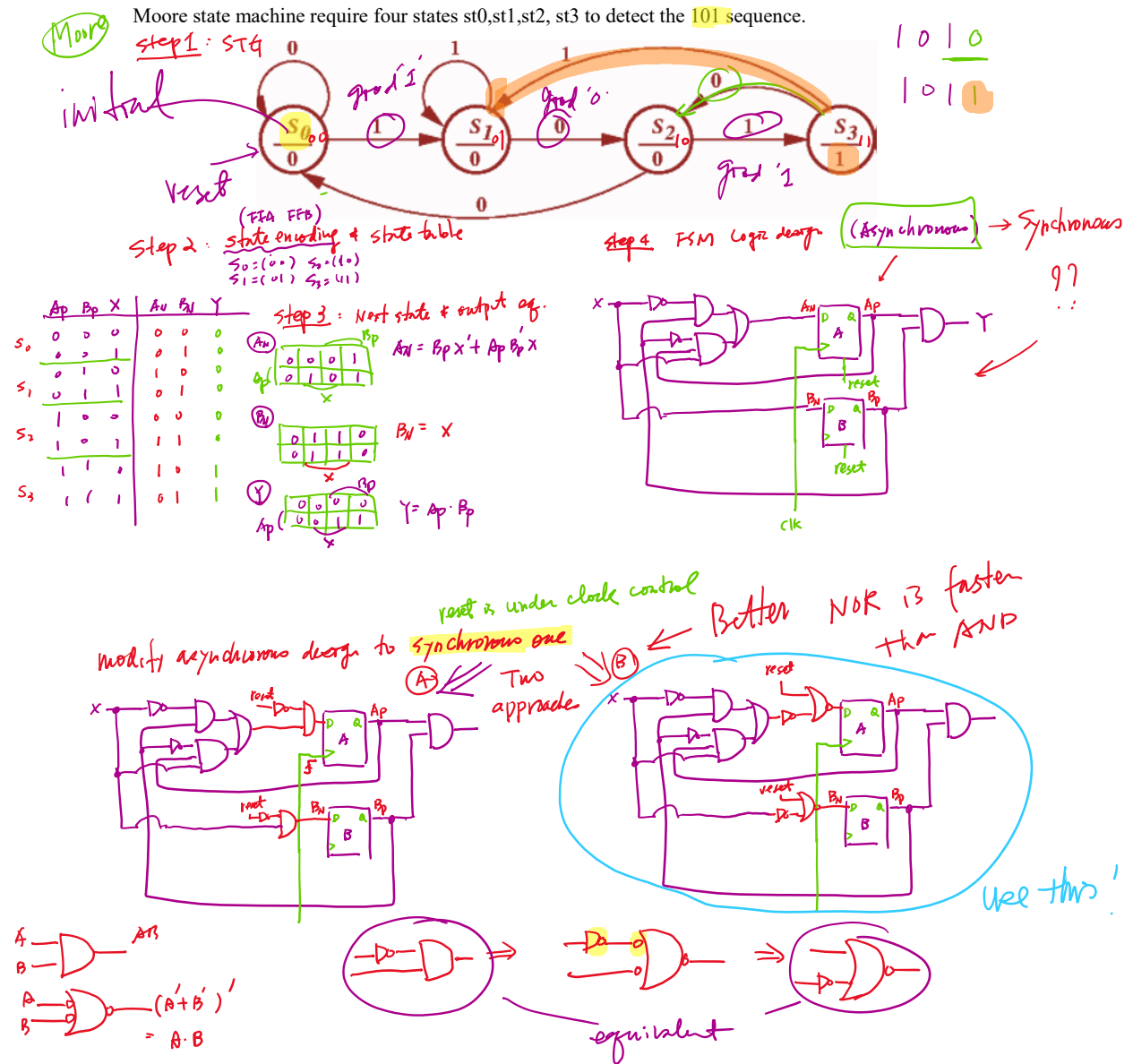


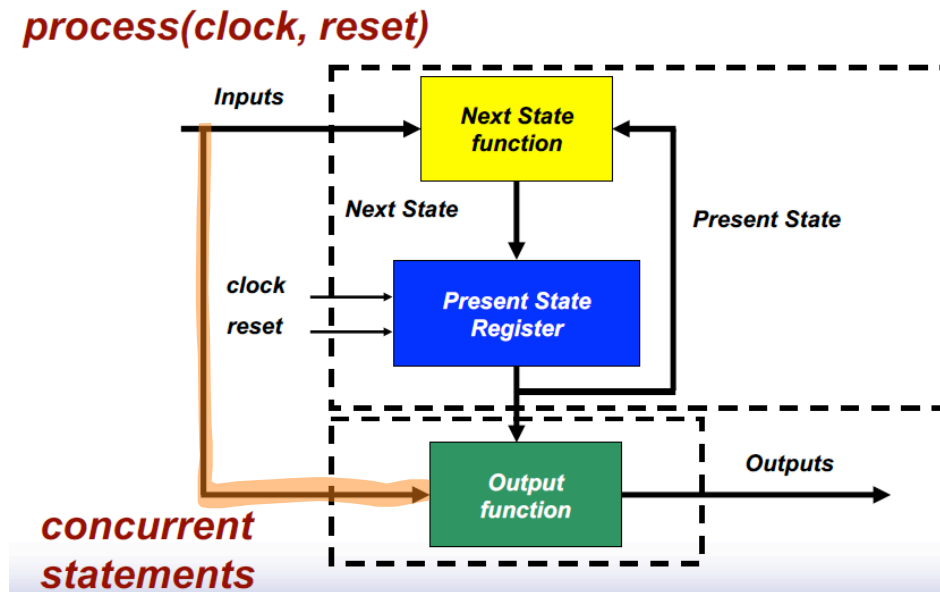B. Mealy machine 101

Let's construct the sequence detector for the sequence 101 using Mealy state machine. The output of the state machine depends on both present state and current input. When the input changes, the output of the state machine updated without waiting for change in clock input.



 Mealy state machine require only three states s_0, s_1, s_2 to detect the 101 sequence.



VHDL code for Sequence detector (101) using Mealy state machine

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```


```
entity mealy is
Port ( clk : in STD_LOGIC;
      din : in STD_LOGIC;
      rst : in STD_LOGIC;
      dout : out STD_LOGIC);
end mealy;
```

architecture Behavioral of mealy is

type state is (st0, st1, st2);

signal present_state, next_state : state;

begin

 

begin

case (present_state) is

when st0 =>

if (din = '1') then

next_state <= st1;

d_out <= '0';

else

next_state <= st0;

d_out <= '0';

end if;

when st1 =>

if (din = '1') then

next_state <= st1;

d_out <= '0';

else

next_state <= st2;

d_out <= '0';

end if;

when st2 =>

if (din = '1') then

next_state <= st1;

d_out <= '1';

else

next_state <= st0;

d_out <= '0';

end if;

when others =>

next_state <= st0;

d_out <= '0';

end case;

end process;

synchronous_process: process(clk)

begin

```
    if (clk = '1' AND clk'event) then
        if (rst = '1') then
            present_state <= st0;
        else
            present_state <= next_state;
        end if;
    end if;
end process;

end Behavioral;
```