 


Q: Complete VHDL code that implements the 8:1 MUX shown in below.



The CE input is a chip enable. When CE = '1', the output acts like the MUX. For example, if SEL = 111 then Data_in[7] is assigned to F_CTRL and if SEL = 001 then Data_in[1] is assigned to F_CTRL. When CE is '0', the output of the MUX is '0'.

a) Use as many “if” statements as you deem necessary to implement your design.

```
library ieee;
use ieee.std_logic_1164.all;
entity mux_8t1_ce is
  port ( Data_in : in std_logic_vector (7 downto 0);
        SEL : in std_logic_vector (2 downto 0);
        CE : in std_logic;
        F_CTRL : out std_logic);
end mux_8t1_ce;

architecture my_8t1_mux of mux_8t1_ce is
  begin
    my_proc: process ( Data_in, SEL, CE )
    begin
```

```
end process my_proc;  
end my_8t1_mux;
```

- b) Use “**case**” statement to implement the 8:1 MUX.

```
library ieee;  
use ieee.std_logic_1164.all;  
entity mux_8t1_ce is  
port ( Data_in : in std_logic_vector (7 downto 0);  
      SEL : in std_logic_vector (2 downto 0);  
      CE : in std_logic;  
      F_CTRL : out std_logic);  
end mux_8t1_ce;
```

```
architecture my_case_ex of mux_8t1_ce is  
begin  
my_proc: process ( SEL,Data_in, CE)  
begin
```

```
end process my_proc;  
end my_8t1_mux;
```