 


1.

a) The graphical symbol and truth table of a 2-to-4 decoder is shown below.

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0



(a) Truth table

(b) Graphical symbol

Complete the behavioral VHDL of 2-to-4 decoder (entity named **dec2to4**) using **IF-THEN-ELSE only**.

```

ENTITY dec2to4 IS
    PORT ( w : IN STD LOGIC VECTOR(1 DOWNTO 0) ;
           En : IN STD LOGIC ;
           y : OUT STD LOGIC VECTOR(0 TO 3) ) ;
END dec2to4 ;

```

ARCHITECTURE Behavior OF **dec2to4** IS

BEGIN


--- use **IF-THEN-ELSE only** ---

END Behavior ;

b) The graphical symbol and truth table of a 2-to-4 decoder is shown below.

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

Complete the behavioral VHDL of 2-to-4 decoder (entity named **dec2to4**) using IF and then **CASE**.

```

ENTITY dec2to4 IS
    PORT ( w : IN STD LOGIC VECTOR(1 DOWNTO 0) ;
           En : IN STD LOGIC ;
           y : OUT STD LOGIC VECTOR(0 TO 3) ) ;
END dec2to4 ;

```


ARCHITECTURE Behavior OF **dec2to4** IS

BEGIN

--- use IF and then **CASE** ----

END Behavior ;

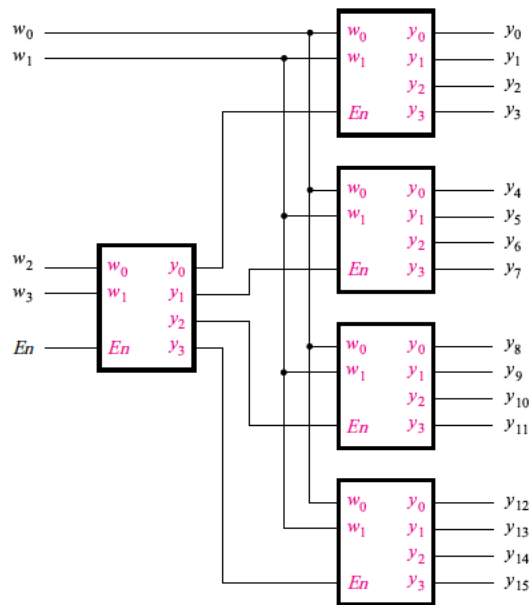c) Complete the behavioral VHDL of 4-to-16 decoder (entity named **dec4to16**).



```
ENTITY dec4to16 IS
    PORT ( w : IN STD LOGIC VECTOR(3 DOWNT0 0) ;
           En : IN STD LOGIC ;
           y : OUT STD LOGIC VECTOR(0 TO 15) ) ;
END dec4to16 ;
```

ARCHITECTURE Structure OF **dec4to16** IS

---- component declaration -----

```
COMPONENT dec2to4
    PORT ( w : IN STD LOGIC VECTOR(1 DOWNT0 0) ;
           En : IN STD LOGIC ;
           y : OUT STD LOGIC VECTOR(0 TO 3) ) ;
END COMPONENT ;
```

---- signal declaration -----

```
SIGNAL m : STD LOGIC VECTOR(0 TO 3) ;
```

```
BEGIN
```

```
END Structure ;
```