
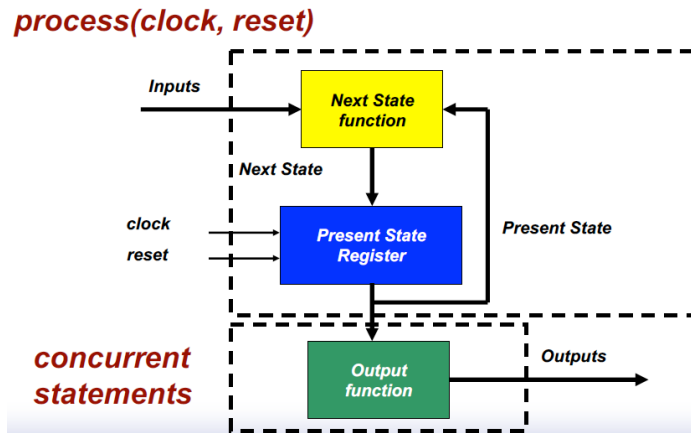


 1. Let's construct the sequence detector for the sequence 3 or more consecutive 1's using **Moore** state machine. The Output of the State machine depends only on present state. The output of state machine are only updated at the clock edge. *The FSM uses an "asynchronous" positive reset which has a higher priority than the clock.*



The Moore state machine require **four states a, b, c, and d** to detect the 3 or more consecutive 1's sequence.

- a) Draw the state transition graph (STG).



Moore

4 states

- b) Complete the entity and architecture pair of VHDL description for the Moore machine.

```
library ieee;
use ieee.std_logic_1164.all;
entity seq_detect is
    port (clk, reset, x : in std_logic;
          y : out std_logic);
end;
```

```
architecture enum of seq_detect is
    type state is (state_a, state_b, state_c, state_d);
```

```
    signal present_state, next_state : state;
```


```
begin
```

```
    nx_state: process (present_state, x) -- next state process
    begin
```

```
        -- use CASE and then IF statement
```

```
        case present_state is
```

Mealy

 

3 states

Flip-Flop A, B

A = (00), B = (01), C = (10)


	A _p	B _p	X	A _n	B _n	Y
A	0	0	0	0	0	0
	0	0	1	0	1	0
B	0	1	0	0	0	0
	1	0	0	0	0	0
C	1	0	1	1	0	1
	1	1	0	X	X	X
	1	1	1	X	X	X

	A _p	B _p	X	A _n	B _n	Y
A	0	0	0	0	0	0
	0	1	0	0	0	0
B	0	1	1	0	0	0
	1	0	0	0	0	0
C	1	0	1	1	0	1
	1	1	0	X	X	X
	1	1	1	X	X	X

	A _p	B _p	X	A _n	B _n	Y
A	0	0	0	0	0	0
	0	1	0	0	0	0
B	0	1	1	0	0	0
	1	0	0	0	0	0
C	1	0	1	1	0	1
	1	1	0	X	X	X
	1	1	1	X	X	X

	A _p	B _p	X	A _n	B _n	Y
A	0	0	0	0	0	0
	0	1	0	0	0	0
B	0	1	1	0	0	0
	1	0	0	0	0	0
C	1	0	1	1	0	1
	1	1	0	X	X	X
	1	1	1	X	X	X

Y = A_p X

 

```

when state_a =>
    if x = '1' then
        next_state <= state_b;
    else
        next_state <= state_a;
    end if;
when state_b =>
    if x = '1' then
        next_state <= state_c;
    else
        next_state <= state_a;
    end if;
when state_c =>
    if x = '1' then
        next_state <= state_d;
    else
        next_state <= state_a;
    end if;
when state_d =>
    if x = '1' then
        next_state <= state_d;
    else
        next_state <= state_a;
    end if;
end case;
end process nx_state;

state_reg: process (clk, reset_bar)    -- state register process
begin
    if (reset = '1') then
        present_state <= state_a;
    elsif (clk'EVENT AND clk = '1') then
        present_state <= next_state;
    end if;


end process state_reg;

-- Concurrent VHDL for output assignment

y <= '1' WHEN (present_state = state_d) ELSE '0';

end enum;
```

 c) Construct **state table** for the Moore machine. There are 4 states, a, b, c, and d. You need 2 flip-flops, A and B for implementation. Use state assignment (A B) = (0 0) for state **a**, (0 1) for state **b**, (1 0) for state **c**, and (1 1) for state **d**. Note: In your state table, use A_P for the present state A, B_P for the present state B, A_N for the next state A, B_N for the next state B, x for the input, and y for the output. **Derive Boolean equation for the next state A_N , B_N , and the output y .**



Moore

A_P	B_P	x	A_N	B_N	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Boolean Equations:

$$A_N = A_P x + B_P x$$

$$B_N = A_P x + B_P' x$$

$$y = A_P B_P$$
