 


Q: Complete VHDL code that implements the 8:1 MUX shown in below.



The CE input is a chip enable. When CE = '1', the output acts like the MUX. For example, if SEL = 111 then Data_in[7] is assigned to F_CTRL and if SEL = 001 then Data_in[1] is assigned to F_CTRL. When CE is '0', the output of the MUX is '0'.

a) Use as many “if” statements as you deem necessary to implement your design.

```

library ieee;
use ieee.std_logic_1164.all;
entity mux_8t1_ce is
port ( Data_in : in std_logic_vector (7 downto 0);
      SEL : in std_logic_vector (2 downto 0);
      CE : in std_logic;
      F_CTRL : out std_logic);
end mux_8t1_ce;

architecture my_8t1_mux of mux_8t1_ce is
begin
my_proc: process ( Data_in, SEL, CE )
begin
    if (CE = '0') then
        F_CTRL <= '0';
    else
        if (SEL = "111") then F_CTRL <= Data_in(7);
        elsif (SEL = "110") then F_CTRL <= Data_in(6);
        elsif (SEL = "101") then F_CTRL <= Data_in(5);
        elsif (SEL = "100") then F_CTRL <= Data_in(4);
        elsif (SEL = "011") then F_CTRL <= Data_in(3);
        elsif (SEL = "010") then F_CTRL <= Data_in(2);
        elsif (SEL = "001") then F_CTRL <= Data_in(1);
        elsif (SEL = "000") then F_CTRL <= Data_in(0);
        else F_CTRL <= '0';
        end if;
    end if;
end process my_proc;
end my_8t1_mux;
  
```

b) Use “case” statement to implement the 8:1 MUX.

```

library ieee;
use ieee.std_logic_1164.all;
entity mux_8t1_ce is
  
```

```

port ( Data_in : in std_logic_vector (7 downto 0);
SEL : in std_logic_vector (2 downto 0);
CE : in std_logic;
F_CTRL : out std_logic);
end mux_8t1_ce;

architecture my_case_ex of mux_8t1_ce is
begin
my_proc: process ( SEL,Data_in, CE)
begin
    if (CE = '1') then
        case (SEL) is
            when "000" => F_CTRL <= Data_in(0);
            when "001" => F_CTRL <= Data_in(1);
            when "010" => F_CTRL <= Data_in(2);
            when "011" => F_CTRL <= Data_in(3);
            when "100" => F_CTRL <= Data_in(4);
            when "101" => F_CTRL <= Data_in(5);
            when "110" => F_CTRL <= Data_in(6);
            when "111" => F_CTRL <= Data_in(7);
            when others => F_CTRL <= '0';
        end case;
    else
        F_CTRL <= '0';
    end if;
end process my_proc;
end my_8t1_mux;

```