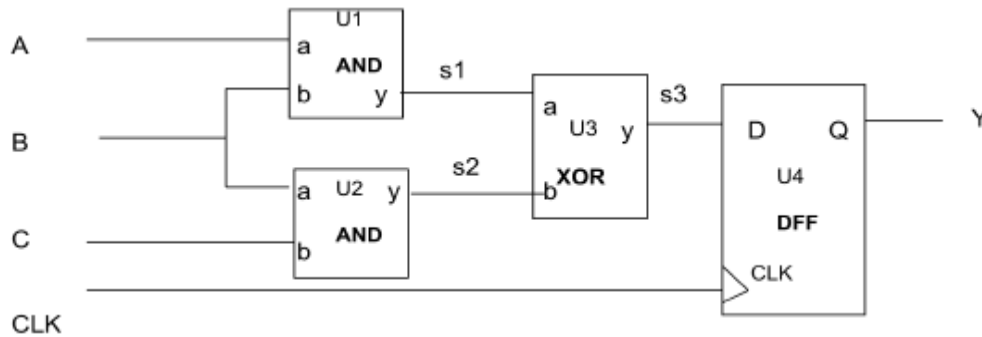


Q1	30 pts		Q3	20 pts		Q5	30 pts		Total	170 pts	
Q2	20 pts		Q4	30 pts		Q6	40 pts (incl. Bonus 20 pts)				

1. [30 pts] Complete the entity and architecture pair of VHDL structural description for a structural representation of a “top_level” circuit shown below. You need to declare the components (i.e., **AND2** for 2-input AND gate, **XOR2** for 2-input XOR gate, and **DFF1** for D flip-flop) used in the schematic diagram. Assume these basic components have been compiled. Ensure all signals and ports of **STD_LOGIC** type and labeled in the schematic diagram match your VHDL code. Use **BY-NAME** method of port mapping.



```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
ENTITY top_level IS
```

```
    PORT (A, B, C, clk : in std_logic;
          Y : out std_logic);
```

```
END ENTITY top_level;
```

```
    architecture structure of top_level is
        -- Component and signal declarations
```

```
        component AND2
            port (a, b: in std_logic;
                  y: out std_logic);
        end component;
        component XOR2
            port (a,b: in std_logic;
                  y: out std_logic);
        end component;
        component DFF1
            port (d, clk: in std_logic;
                  q: out std_logic);
        end component;
```

```
        signal s1, s2, s3: std_logic
```

```
    begin
        -- Component instantiations statements
```

```
        u1: AND2
            port map (a=>A, b=>B, y=>s1);
        u2: AND2
            port map (a=>B, b=>C, y=>s2);
        u3: XOR2
            port map (a=>s1, b=>s2, y=>s3);
        u4: DFF1
            port map (d=>s3, clk=>clk, q=>Y);
```

```
    end structure;
```

2. [20 pts] The VHDL compiler has found multiple errors with the following code. **Identify at least 10 errors.** Identifying non errors will result in a loss of 2 points. **Write your corrected line # and VHDL code on the right column.**

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.all;
3. entity decoder1
4.     port(a : in BIT(1 downto 0);
5.          EN: in BIT;
6.          b : out BIT(3 downto 0));
7. end decoder1;
8.
9. architecture bhv of decoder1
10. begin
11. process(a, EN)
12. begin
13.     if (EN = 0) then
14.         if (a="00") then
15.             b = "0001";
16.         else (a="01") then
17.             b = "0010";
18.         else (a="10") then
19.             b = "0100";
20.         else
21.             b = "1000";
22.         end if;
23.     else
24.         if (a="00") then
25.             b = "1011";
26.         else (a="01") then
27.             b = "1111";
28.         else (a="10") then
29.             b = "0100";
30.         else
31.             b = "1100";
32.         end if;
33.     end if;
34. end;
35. end bhv;

```

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.all;
3. entity decoder1 is
4.     port(a : in BIT_VECTOR (1 downto 0);
5.          EN: in BIT;
6.          b : out BIT_VECTOR (1 downto 0));
7. end decoder1;
8.
9. architecture bhv of decoder1 is
10. begin
11. process(a, EN)
12. begin
13.     if (EN = '0') then
14.         if (a="00") then
15.             b <= "0001";
16.         elsif (a="01") then
17.             b <= "0010";
18.         elsif (a="10") then
19.             b <= "0100";
20.         else
21.             b <= "1000";
22.         end if;
23.     else
24.         if (a="00") then
25.             b <= "1011";
26.         elsif (a="01") then
27.             b <= "1111";
28.         elsif (a="10") then
29.             b <= "0100";
30.         else
31.             b <= "1100";
32.         end if;
33.     end if;
34. end process;
35. end bhv;


```

3. [20 pts] Continue Prob. 2


a) [10 pts] After fixing errors of the entity decoder, construct the truth table in the following format.

Input			Output			
EN	a(1)	a(0)	b(3)	b(2)	b(1)	b(0)
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0
1	0	0	1	0	1	1
1	0	1	1	1	1	1
1	1	0	0	1	0	0
1	1	1	1	1	0	0

 
b) [10 pts] Use K-maps to derive the optimal Boolean expression for b(3), b(2), b(1), and b(0).



 
$$b(3) = EN \cdot a(1)' + a(1) \cdot a(0)$$


 
$$b(2) = EN \cdot a(0) + a(1) \cdot a(0)'$$


 
$$b(1) = EN \cdot a(1)' + a(1) \cdot a(0)$$



$$b(0) = EN \cdot a(1)' + a(1) \cdot a(0)'$$

4. [30 pts] Complete VHDL that implements two functions: $F(A,B,C) = B + A'C'$ and $G(A,B,C) = AB' + C$
- a) [10 pts] Use **concurrent VHDL code** (use the exact Boolean expression $F(A,B,C) = B + A'C'$ and $G(A,B,C) = AB' + C$)

```

entity function is
    port ( A,B,C : in std_logic;
           F,G : out std_logic);
end function;

architecture concurrent of function is
begin
    F <= B OR (NOT A AND NOT C);
    G <= (A AND NOT B) OR C;
end concurrent;

```

- b) [10 pts] Use **if** statement (use the exact Boolean expression $F(A,B,C) = B + A'C'$ and $G(A,B,C) = AB' + C$)

```

entity function is
    port ( A,B,C : in std_logic;
           F,G : out std_logic);
end function;

architecture behavior_1 of function is
begin
    proc1: process(A,B,C)

        begin

            if (B = '1') then
                F <= '1';
            elsif (A = '0' and C = '0') then
                F <= '1';
            else
                F <= '0';
            end if;

            if (A = '1' and B = '0') then
                G <= '1';
            elsif (C = '1') then
                G <= '1';
            else
                G <= '0';
            end if;

        end process proc1;
    end behavior_1;

```

c) [10 pts] Complete VHDL that implements two functions: $F(A,B,C) = B + A'C'$ and $G(A,B,C) = AB' + C$

Use **case** statement. Note: *Use two case statements; one for F and the other for G.*

```
entity function is
    port ( A,B,C : in std_logic;
           F,G : out std_logic);
end function;

architecture behavior_2 of function is

    signal ABC: std_logic_vector(2 downto 0);
begin
    ABC <= (A,B,C);
    my_proc: process (ABC)
    begin
        case (ABC) is
            when "000" => F <= '1';
            when "010" => F <= '1';
            when "011" => F <= '1';
            when "110" => F <= '1';
            when "111" => F <= '1';
            when others => F <= '0';
            end case;

            case (ABC) is
            when "001" => G <= '1';
            when "011" => G <= '1';
            when "100" => G <= '1';
            when "101" => G <= '1';
            when "111" => G <= '1';
            when others => G <= '0';
            end case;
        end process my_proc;
    end behavior_2;
```

5. [30 pts] Complete the waveform for the output **q** for the following different architectures of D flip-flop.



```

ENTITY dff_reset IS
  PORT (reset, clk: IN BIT;
        d: IN STD_LOGIC;
        q: OUT STD_LOGIC);
END ENTITY dff_reset;


```

- a) [15 pts] ARCHITECTURE a_behavior OF dff_reset IS
 BEGIN
 PROCESS (clk)
 BEGIN
 IF (clk'EVENT AND clk = '0') THEN
 IF (reset = '1') THEN
 q <= '0';
 ELSE
 q <= d;
 END IF;
 END IF;
 END PROCESS;
 END ARCHITECTURE a_behavior;

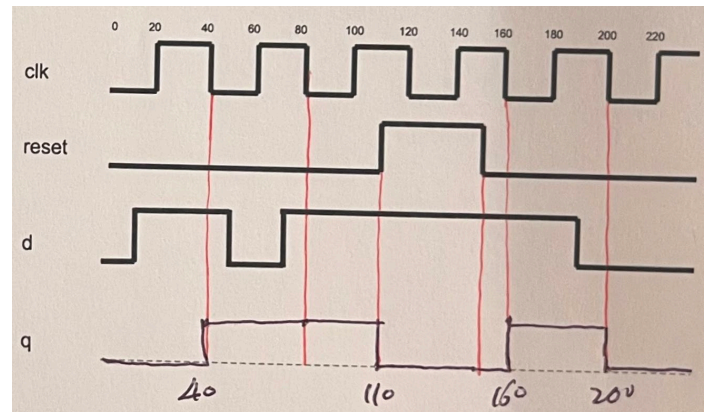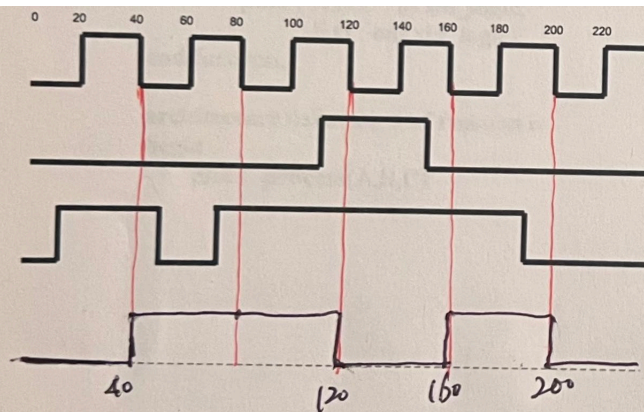- b) [15 pts] ARCHITECTURE b_behavior OF dff_reset IS
 BEGIN
 PROCESS (clk, reset)
 BEGIN
 IF (reset = '1') THEN
 q <= '0';
 ELSIF (clk'EVENT AND clk = '0') THEN
 q <= d;
 END IF;
 END PROCESS;
 END ARCHITECTURE b_behavior;



 6. [40 pts] Below is a state diagram for a Moore FSM implementation. The Output of the State machine depends only on present state. *The FSM uses a synchronous **negative** reset input, `reset_bar` and **clock has a higher priority than negative reset**.*



a) [20 pts] Complete the architecture of VHDL **behavioral** description below.

```

library ieee;
use ieee.std_logic_1164.all;
entity seq_detect is
    port (clk, reset_bar, x : in std_logic;
          y : out std_logic);
end;

architecture enum of seq_detect is
    type state is (state_a, state_b, state_c, state_d);

    signal present_state, next_state : state;

begin

    nx_state: process (present_state, x) -- next state process
    begin
        -- use CASE and then IF statement
        case present_state is
            when state_a =>
                if x = '1' then
                    next_state <= state_b;
                else
                    next_state <= state_a;
                end if;
            when state_b =>
                if x = '0' then
                    next_state <= state_c;
                else
                    next_state <= state_b;
                end if;
            when state_c =>
                if x = '1' then
                    next_state <= state_d;
                else
                    next_state <= state_a;
                end if;
        end case;
    end process nx_state;

```

```

                                when state_d =>
                                    if x = '0' then
                                        next_state <= state_c;
                                    else
                                        next_state <= state_b;
                                    end if;
                                end case;
                            end process nx_state;

state_reg: process (clk, reset_bar)    -- state register process
begin
-- Synchronous reset; clock has a higher priority than negative reset
if (clk'EVENT AND clk = '1') then
    if (reset_bar = '0') then
        present_state <= state_a;
    else
        present_state <= next_state;
    end if;
end if;
end process state_reg;

-- Concurrent VHDL for output assignment
y <= '1' WHEN present_state = state_d ELSE '0';

end enum;

```

b) [Bonus 20 pts] Construct state table for the Moore machine. There are 4 states, a, b, c and d. You need 2 flip-flops, A and B for implementation. Use state assignment (A B) = (0 0) for state a, (0 1) for state b, (1 0) for state c, and (1 1) for state d. Note: In your state table, use A_p for the present state A, B_p for the present state B, A_N for the next state A, B_N for the next state B, x for the input, and y for the output. Derive Boolean equation for A_N , B_N , and y.

A_p	B_p	x	A_N	B_N	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	0	1	1

(A_N)

	A_p	0	1
B_p	0	0	1
	1	1	0

x

$A_N = B_p \bar{x} + A_p \bar{B}_p x$

(B_N)

	A_p	0	1
B_p	0	1	0
	1	1	0

x

$B_N = x$

④

			B_p
	0	0	0
A_p	0	0	1
			1

x

$$y = A_p \cdot B_p$$