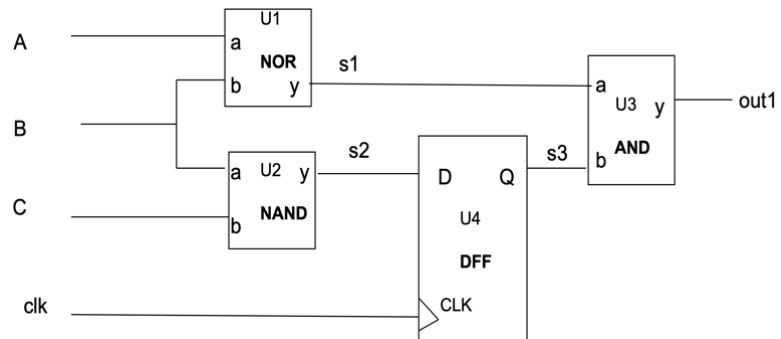


1. [20 pts] Complete the entity and architecture pair of VHDL structural description for a structural representation of a “top_level” circuit shown below. You need to declare the components (i.e., **NAND** for 2-input NAND gate, **AND** for 2-input AND gate, **NOR** for 2-input NOR gate, and **DFF** for D flip-flop) used in the schematic diagram. Assume these basic components have been compiled. Ensure all signals and ports of **STD_LOGIC** type and labeled in the schematic diagram match your VHDL code. Use **BY-NAME** method of port mapping.



```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
ENTITY top_level IS

```

```

END ENTITY top_level;

```

```

    architecture structure of top_level is
        -- Component and signal declarations

```

```

    begin
        -- Component instantiations statements

```

end structure;

2. [20 pts] The VHDL compiler has found multiple errors with the following code. Identify 10 errors. Identifying non-errors will result in a loss of 2 points.

Write your corrected VHDL next to the line number.

1. library ieee	1.
2. use ieee.std_logic_1164.all;	2.
3.	3.
4. entity priority is	4.
5. port (x: in std_logic_vector (3 downto 0),	5.
6. a: out std_logic_vector (3 downto 0));	6.
7. end priority;	7.
8.	8.
9. architecture looparch of priority	9.
10. begin	10.
11. p0: process (x)	11.
12.	12.
13. a <= 00;	13.
14. for k in 3 downto 1	14.
15. if x(k) = 0 then	15.
16. a(k) <= 1;	16.
17. elsif	17.
18. a(k) <= 0;	18.
19. end if;	19.
20. end loop;	20.
21.	21.
22. end looparch;	22.

3. [20 pts] Complete VHDL that implements two functions: $F(A,B,C) = AB + B'C'$ and $G(A,B,C) = A'B' + BC$
- a) [6 pts] Use *concurrent VHDL code* (use the exact Boolean expression $F(A,B,C) = AB + B'C'$ and $G(A,B,C) = A'B' + BC$)

```
entity function is
    port ( A,B,C : in std_logic;
           F,G : out std_logic);
end function;
```

```
architecture concurrent of function is
begin
```

```
end concurrent;
```

- b) [7 pts] Use *if* statement (use the exact Boolean expression $F(A,B,C) = AB + B'C'$ and $G(A,B,C) = A'B' + BC$)

```
entity function is
    port ( A,B,C : in std_logic;
           F,G : out std_logic);
end function;
```

```
architecture behavior_1 of function is
begin
    proc1: process(A,B,C)
```

```
        end process proc1;
end behavior_1;
```

c) [7 pts] Complete VHDL that implements two functions: $F(A,B,C) = AB + B'C'$ and $G(A,B,C) = A'B' + BC$

Use *case* statement. Note: *Use two case statements; one for F and the other for G.*


```
entity function is  
    port ( A,B,C : in std_logic;  
           F,G : out std_logic);  
end function;  
  
architecture behavior_2 of function is
```

```
end behavior_2;
```


4. [20 pts] Complete the waveform for the output **q** for the following different architectures of D flip-flop.

```
ENTITY dff_reset IS
  PORT (reset, clk: IN BIT;
        d: IN STD_LOGIC;
        q: OUT STD_LOGIC);
END ENTITY dff_reset;
```

 a) [10 pts] ARCHITECTURE a_behavior OF dff_reset IS
 BEGIN
 PROCESS (clk)
 BEGIN
 IF (clk'EVENT AND clk = '1') THEN
 IF (reset = '1') THEN
 q <= '0';
 ELSE
 q <= d;
 END IF;
 END IF;
 END PROCESS;
 END ARCHITECTURE a_behavior;



 b) [10 pts] ARCHITECTURE b_behavior OF dff_reset IS
 BEGIN
 PROCESS (clk, reset)
 BEGIN
 IF (reset = '1') THEN
 q <= '0';
 ELSIF (clk'EVENT AND clk = '1') THEN
 q <= d;
 END IF;
 END PROCESS;
 END ARCHITECTURE b_behavior;



5. [20 pts] Construct the **truth table**. Use K-maps to derive the sum-of-products for **b(3), b(2), b(1), and b(0)**.


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity decoder1
  port(a : in BIT_VECTOR(1 downto 0);
       EN: in BIT;
       b : out BIT_VECTOR(3 downto 0));
end decoder1;

architecture bhv1 of decoder1 is
begin
  process(a, EN)
  begin
    if (EN = '0') then
      if (a="01") then
        b <= "0010";
      elsif (a="10") then
        b <= "0100";
      else
        b <= "0000";
      end if;
    else
      if (a="00") then
        b <= "0001";
      elsif (a="11") then
        b <= "1000";
      else
        b <= "1111";
      end if;
    end if;
  end process;
end bhv1;
```

 6. [10 pts] Complete the waveform for the output q for the following different architectures of D flip-flop.

```
ENTITY dff_reset IS
  PORT (reset, clk: IN BIT;
        d: IN BIT;
        q: OUT BIT);
END ENTITY dff_reset;
```

```
ARCHITECTURE c_behavior OF dff_reset IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clk'EVENT AND clk = '0') THEN -- Note: Negative-edge trigger.
      IF (reset = '1') THEN
        q <= '0';
      ELSE
        q <= d;
      END IF;
    END IF;
  END PROCESS;
END ARCHITECTURE c_behavior;
```



7. Let's construct the sequence detector for the sequence **010** using **Moore** state machine. The output of the State machine depends only on the present state. The output of state machine is only updated at the clock edge. **The FSM uses a "positive" reset (i.e., $rst = 1$); the clock has a higher priority than the reset. All flip-flops are rising edge-triggered.**

The Moore state machine require **four states *a*, *b*, *c*, and *d*** to detect the **010** sequence. The initial state is **state *a* (*sta*)**.

a) Draw the state transition graph (STG).

Complete the entity and architecture pair of VHDL description for the Moore machine.

```
library ieee;
use ieee.std_logic_1164.all;
entity seq_detect is
    port (clk, reset, x : in std_logic;
          y : out std_logic);
end seq_detect;

architecture enum of seq_detect is
    type state is (sta, stb, stc, std); -- use "sta" to represent 'state a', etc.
    signal present_state, next_state : state;

begin

    nx_state: process (present_state, x) -- next state process
    begin
        -- use CASE and then IF statement
```

b)

```
end process nx_state;
```

```
state_reg: process (clk, reset) -- state register process
begin
```

c)

```
end process state_reg;
```

```
-- Concurrent VHDL for output assignment
```

d)

```
end enum;
```

(e) **Construct state table for the FSM machine.** There are 4 states, sta, stb, stc, and std. You need **2 flip-flops, A and B** for implementation. Use state assignment (A B) = (0 0) for state **sta**, (0 1) for state **stb**, (1 0) for state **stc**, and (1 1) for state **std**. Note: In your state table, use Ap for the present state A, Bp for the present state B, An for the next state A, Bn for the next state B, “x” for the input, and “y” for the output. **Derive Boolean equation for An, Bn, and the output “y”.**

(f) Sketch the FSM logic design.