 


1. Write an entity and architecture pair of VHDL structural description for a structural representation of a circuit sequential_1 shown below. You need to declare the components (i.e., **DFF1** for D flip-flop, **OR2** for 2-input OR gate, **INV1** for inverter gate, and **MUX2** for 2x1 MUX gate) used in the schematic diagram. Assume these basic components have been compiled. Ensure all signals and ports of **STD_LOGIC** type and labeled in the schematic diagram match your VHDL code. Use **BY-NAME** method of port mapping.



```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;
ENTITY sequential_1 IS
    PORT (a, b, c, clk : in std_logic;
          out1 : out std_logic);
END ENTITY sequential_1;
architecture sequential_structure of sequential_1 is

```

-- Component and signal declarations

```

    component INV1
        port (a: in std_logic;
              z: out std_logic);
    end component;
    component OR2
        port (a,b: in std_logic;
              z: out std_logic);
    end component;
    component MUX2
        port (a,b,sel: in std_logic;
              z: out std_logic);
    end component;
    component DFF1
        port (d, clk: in std_logic;
              q: out std_logic);
    end component;

```

-- declaration of signals used to interconnect gates
signal s1, s2, s3: std_logic;

begin

-- Component instantiations statements

```

u1: INV1
    port map (a=>b, z=>s1);
u2: OR2
    port map (a=>b, b=>c, z=>s2);
u3: MUX2
    port map (a=>s1, b=>s2, sel=>a, z=>s3);
u4: DFF1
    port map (d=>s3, clk=>clk, q=>out1);
end sequential_structural;

```