


Pipeline

Pipeline

- Pipeline is an important technique used in (DSP) systems, microprocessors, etc.
- Pipeline results in **speed enhancement** for the **critical path**.
- It can either increase the clock speed or reduce the power consumption at the same speed in a DSP system.
- It increases the throughput of the system when processing a stream of tasks.


$$f_{clk} = 100 \text{ MHz}$$

$$T_{clk} = 10 \text{ (ns)}$$

 


Pipeline

Non-pipeline Adder vs Pipeline Adder

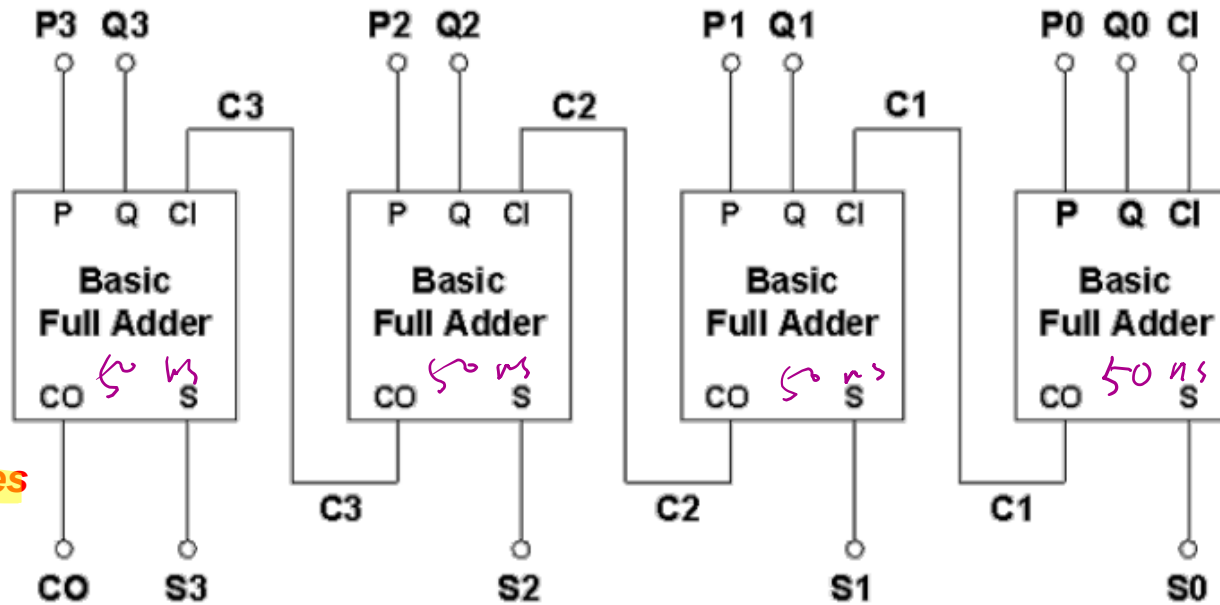

- Insert 4 pipelines
- Insert 2 FF's

Pipeline

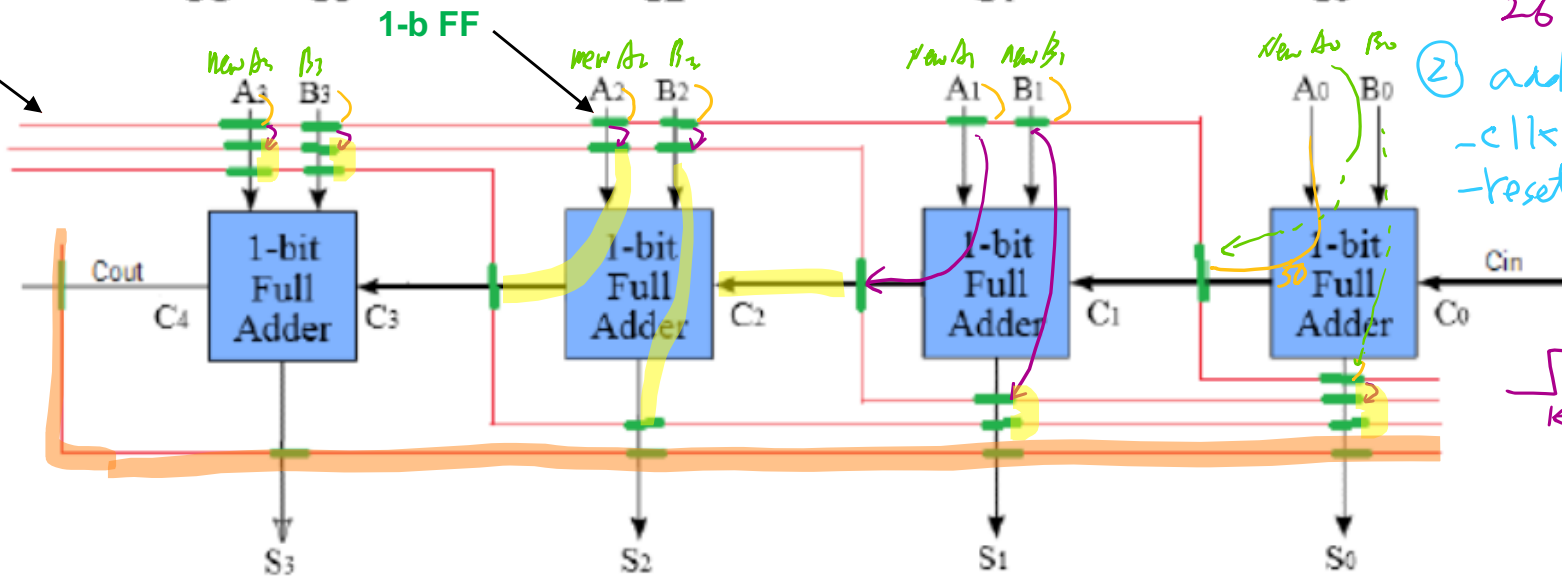


pipeline hardware overhead


① 8
7
6
+ 5


26 D-FF's


② and
-clk
-reset or resetn

 


1st clock

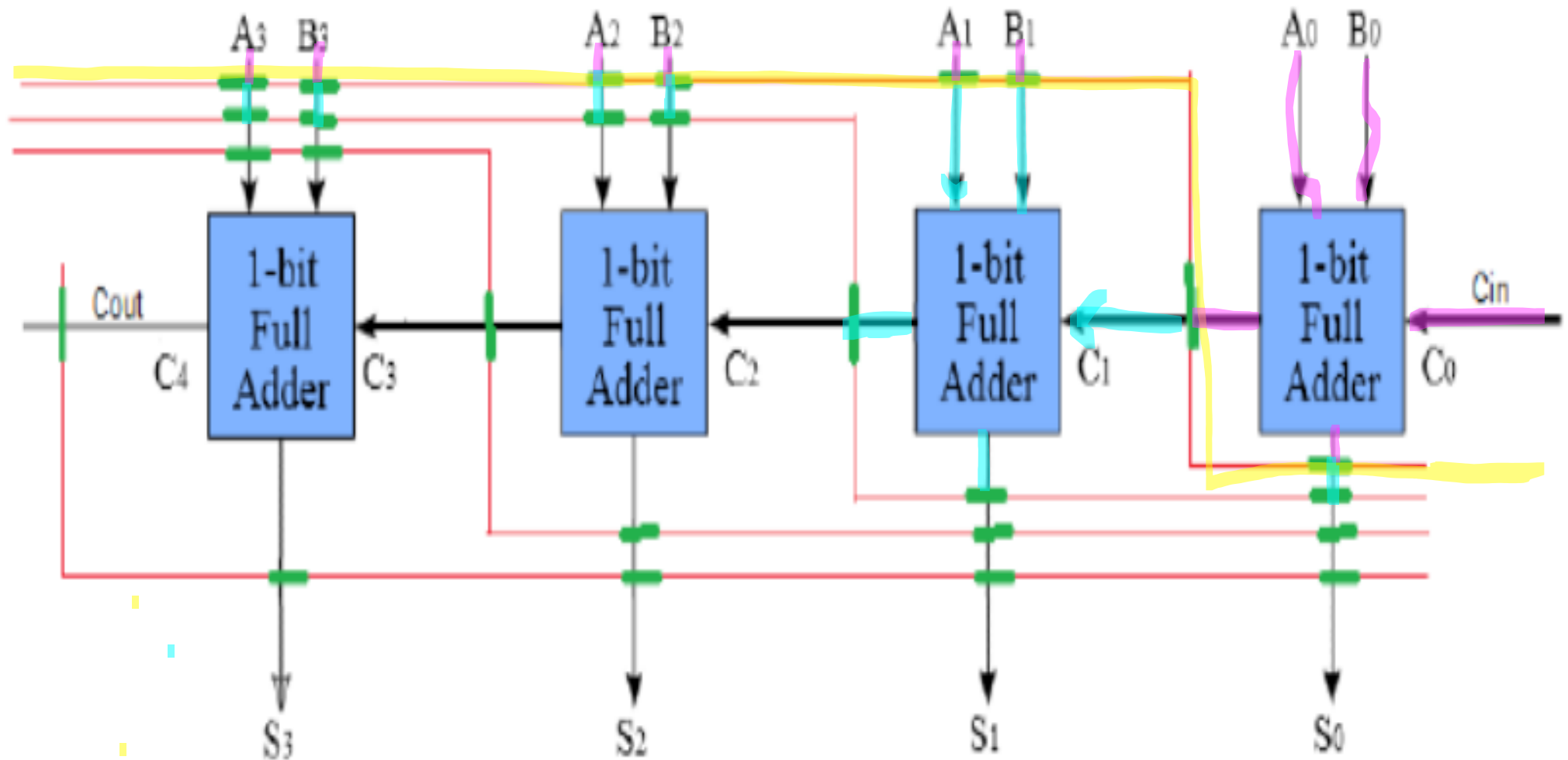

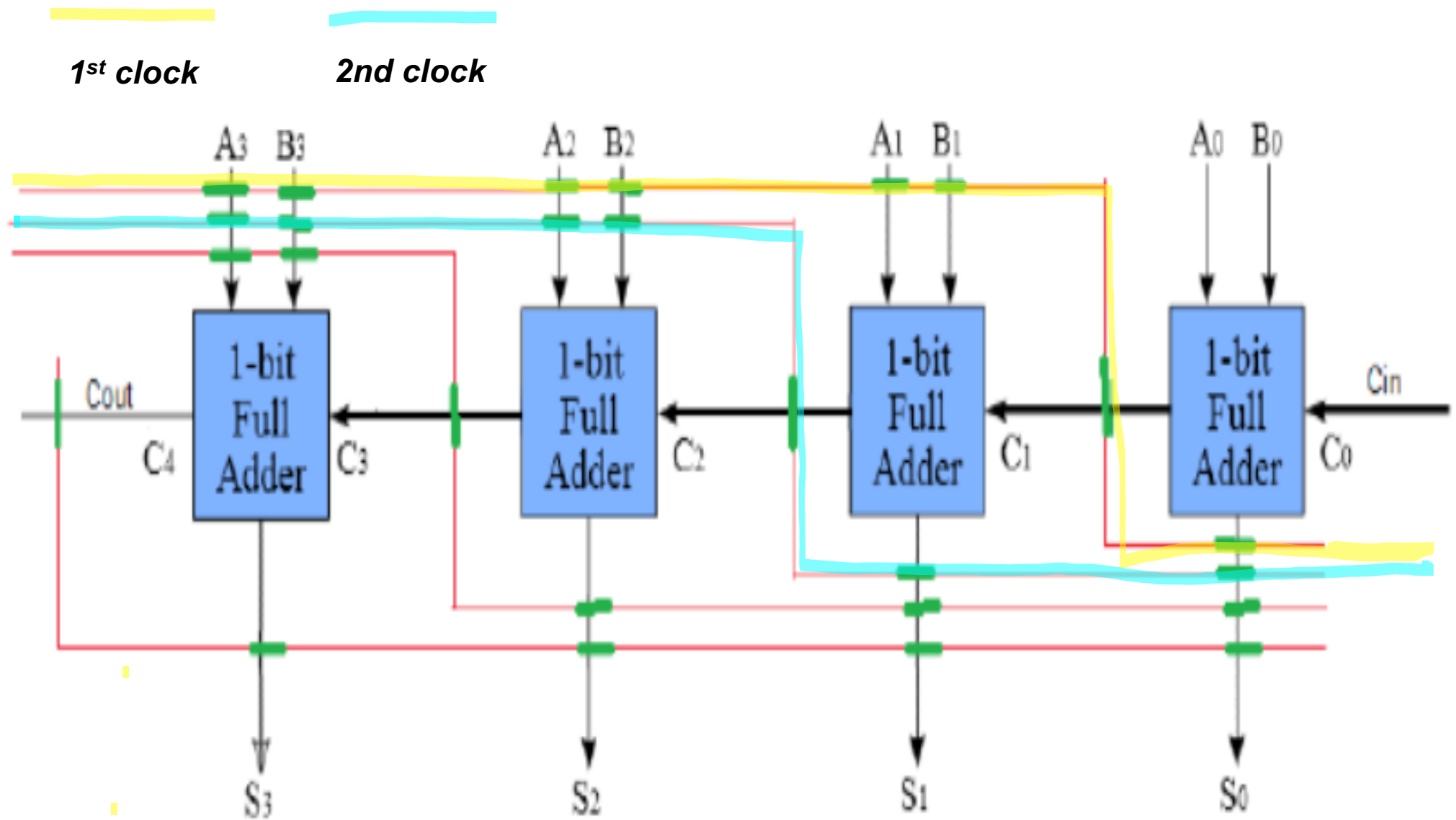


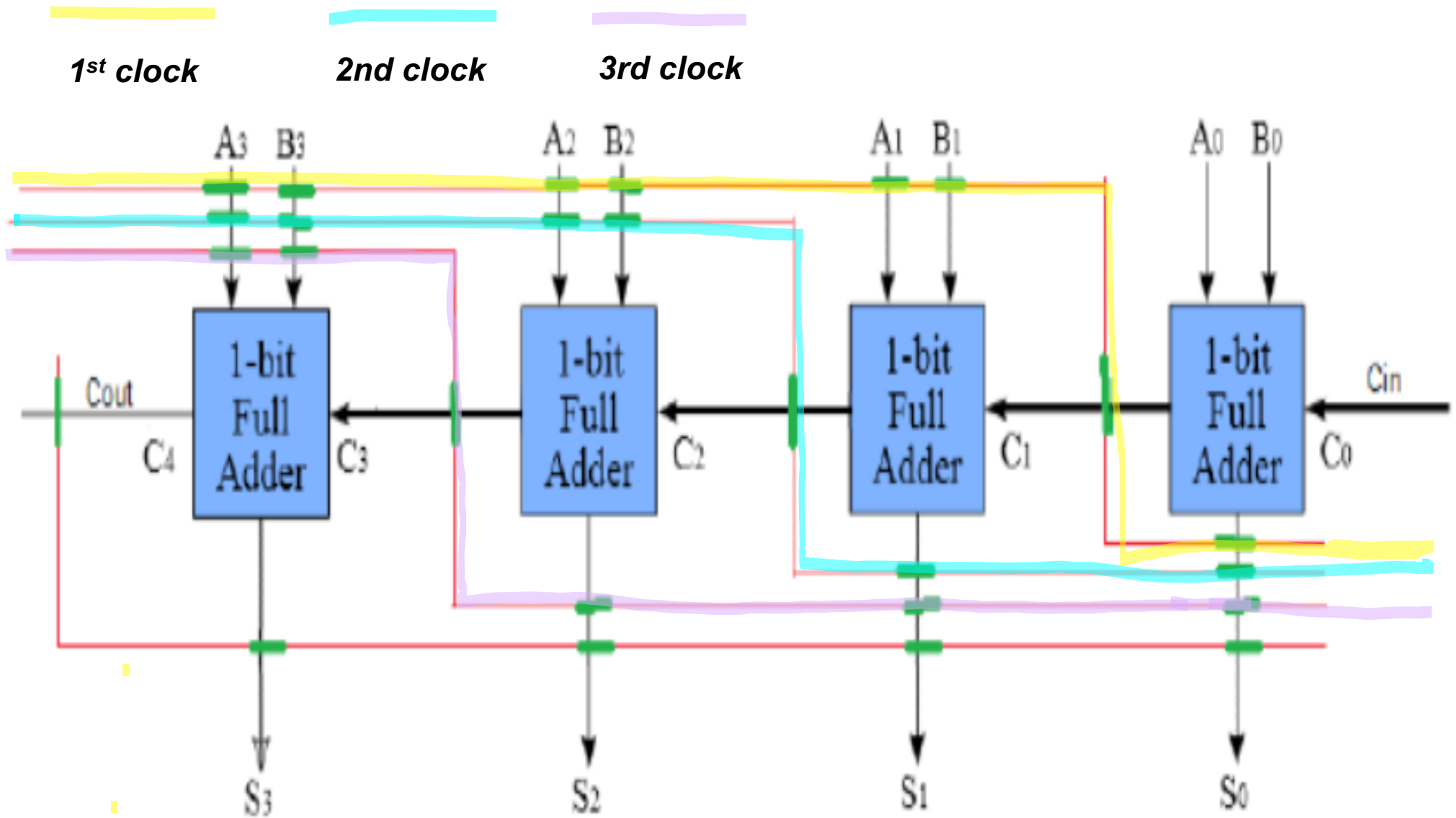

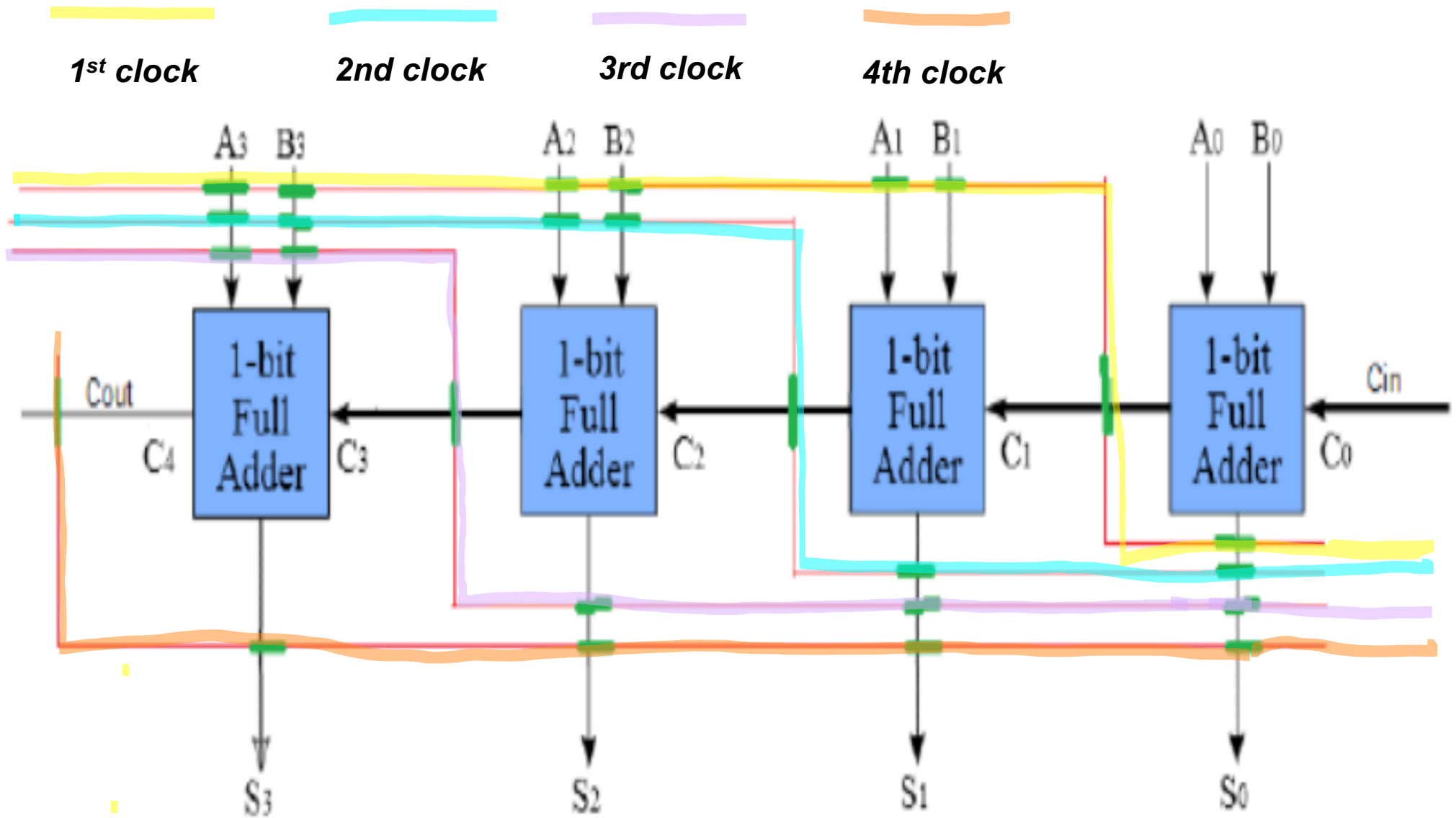


Pipeline

Non-pipeline Adder vs Pipeline Adder

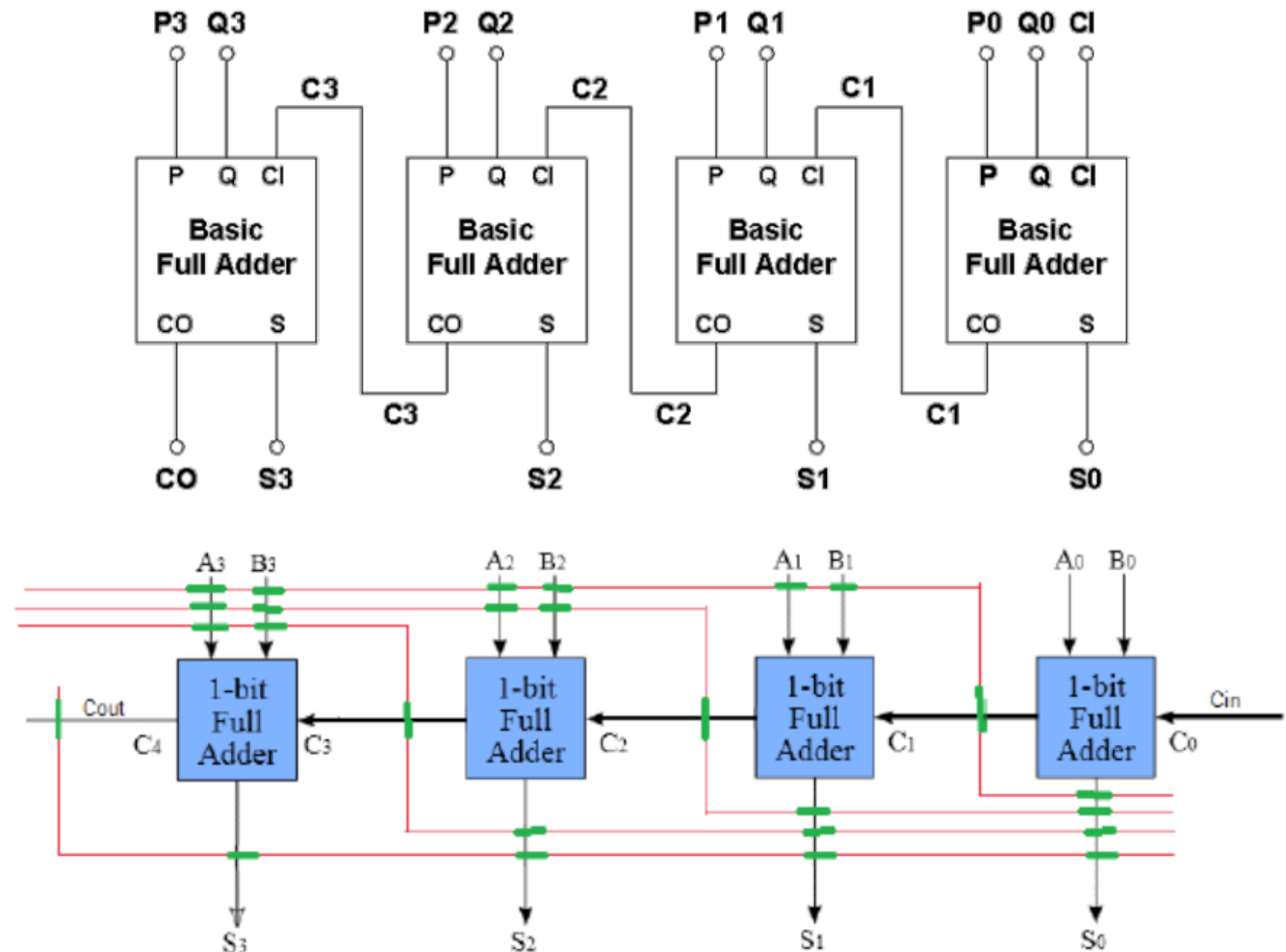

Assume 1-b FA delay is 10 ns.

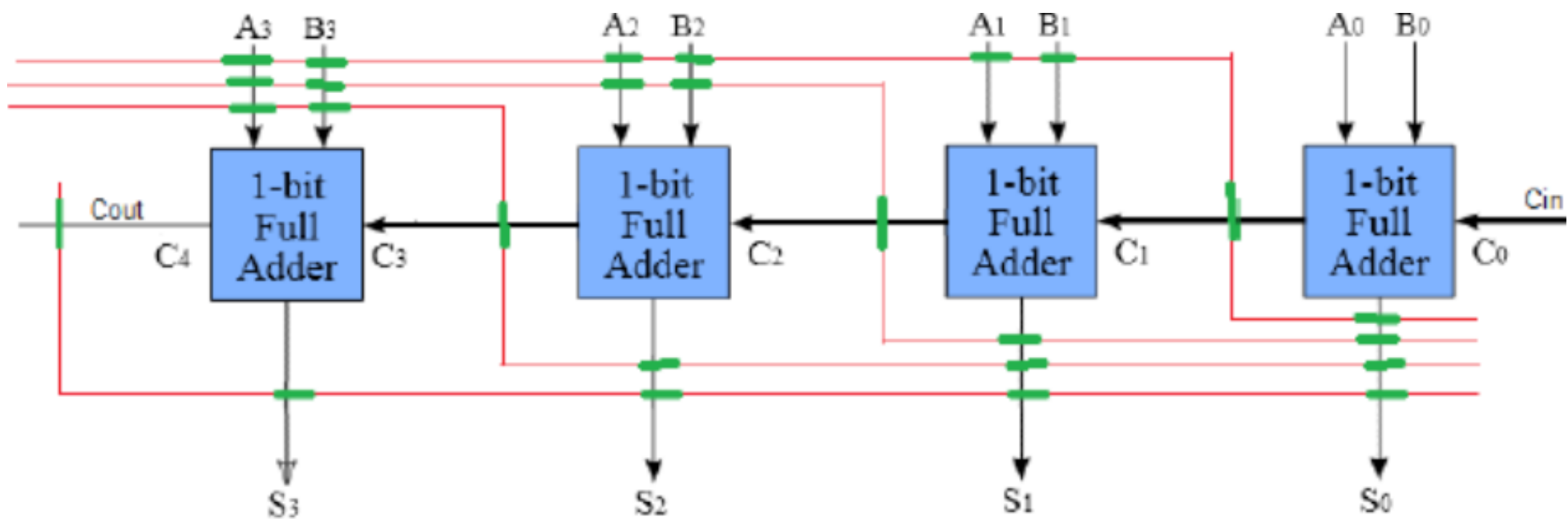- Non-pipeline: It takes 40 ns to complete 4-b addition $\Rightarrow f = 1/T = 1/40\text{ns} = 25 \text{ MHz}$.
- Pipeline: It takes the first 4 clock cycles to generate the first 4-b addition result; thereafter, It generates 4-b addition result every clock cycle. $\Rightarrow f = 1/T = 1/10\text{ns} = 100 \text{ MHz}$.




entity FA is
 PORT (Cin, A, B: IN STD_LOGIC ;
 Cout, S: OUT STD_LOGIC) ;
 END entity;


ARCHITECTURE behaviour OF FA is
 begin
 S <= A XOR B XOR Cin ;
 Cout <= (A AND B) OR (Cin AND A) OR (Cin AND B) ;
 end architecture;

entity reg is
 port(D, CLK, RSTn: in std_logic;
 Q: out std_logic);
 end entity;

 architecture behaviour of reg is
 begin
 process(CLK, RSTn)
 begin
 if RSTn = '0' then
 Q <= '0';
 elsif rising_edge(clk) then
 Q <= D;
 end if;
 end process;
 end architecture;



Handwritten note: CLK is zero and CLK=1

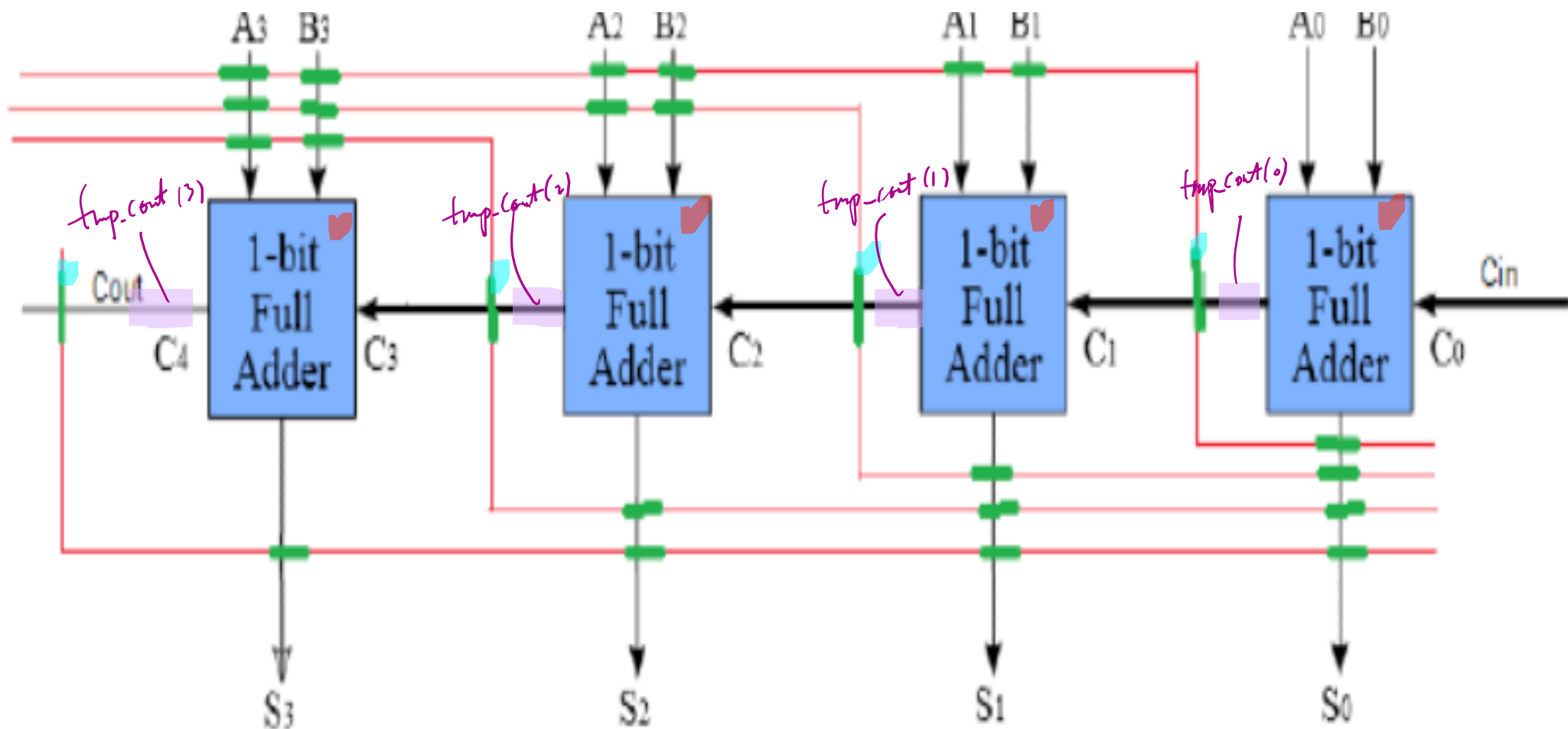

-- Declaration of signals used to interconnect gates

```

signal tmp_cout : std_logic_vector(3 downto 0);
signal tmp_cin : std_logic_vector(2 downto 0);
signal tmp_S0 : std_logic_vector(3 downto 0);
signal tmp_S1 : std_logic_vector(2 downto 0);
signal tmp_S2 : std_logic_vector(1 downto 0);
signal tmp_S3 : std_logic;
signal tmp_A1 : std_logic;
signal tmp_B1 : std_logic;

```

```

reg_cout0: reg port map(tmp_cout(0), CLK, RSTn, tmp_cin(0));
reg_cout1: reg port map(tmp_cout(1), CLK, RSTn, tmp_cin(1));
reg_cout2: reg port map(tmp_cout(2), CLK, RSTn, tmp_cin(2));
reg_cout3: reg port map(tmp_cout(3), CLK, RSTn, Cout);


```

```

FA_0: FA port map(Cin=>Cin, A=>A(0), B=>B(0), S=>tmp_S0(0),
Cout=>tmp_cout(0));
FA_1: FA port map(Cin=>tmp_cin(0), A=>tmp_A1, B=>tmp_B1, S=>tmp_S1(0),
Cout=>tmp_cout(1));
FA_2: FA port map(Cin=>tmp_cin(1), A=>tmp_A2(1), B=>tmp_B2(1),
S=>tmp_S2(0), Cout=>tmp_cout(2));
FA_3: FA port map(Cin=>tmp_cin(2), A=>tmp_A3(2), B=>tmp_B3(2), S=>tmp_S3,
Cout=>tmp_cout(3));

```

port map
by "NAME"

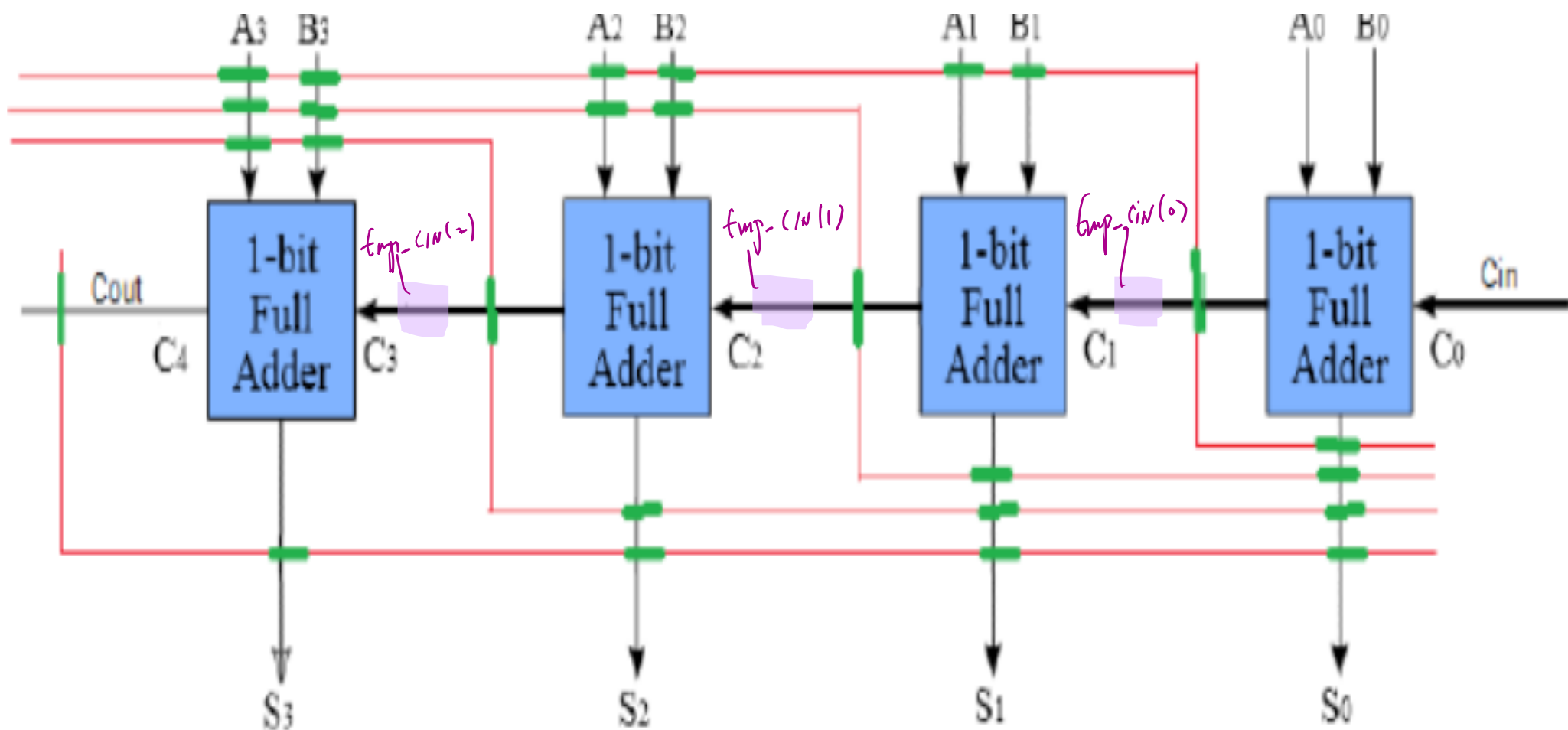


-- Declaration of signals used to interconnect gates

```


signal tmp_cout : std_logic_vector(3 downto 0);
signal tmp_cin : std_logic_vector(2 downto 0);
signal tmp_S0 : std_logic_vector(3 downto 0);
signal tmp_S1 : std_logic_vector(2 downto 0);
signal tmp_S2 : std_logic_vector(1 downto 0);
signal tmp_S3 : std_logic;
signal tmp_A1 : std_logic;
signal tmp_B1 : std_logic;

```


FA_1: FA port map(Cin=>tmp_cin(0), A=>tmp_A1, B=>tmp_B1, S=>tmp_S1(0), Cout=>tmp_cout(1));
FA_2: FA port map(Cin=>tmp_cin(1), A=>tmp_A2(1), B=>tmp_B2(1), S=>tmp_S2(0), Cout=>tmp_cout(2));
FA_3: FA port map(Cin=>tmp_cin(2), A=>tmp_A3(2), B=>tmp_B3(2), S=>tmp_S3, Cout=>tmp_cout(3));
reg_cout0: reg port map(tmp_cout(0), CLK, RSTn, tmp_cin(0));
reg_cout1: reg port map(tmp_cout(1), CLK, RSTn, tmp_cin(1));
reg_cout2: reg port map(tmp_cout(2), CLK, RSTn, tmp_cin(2));

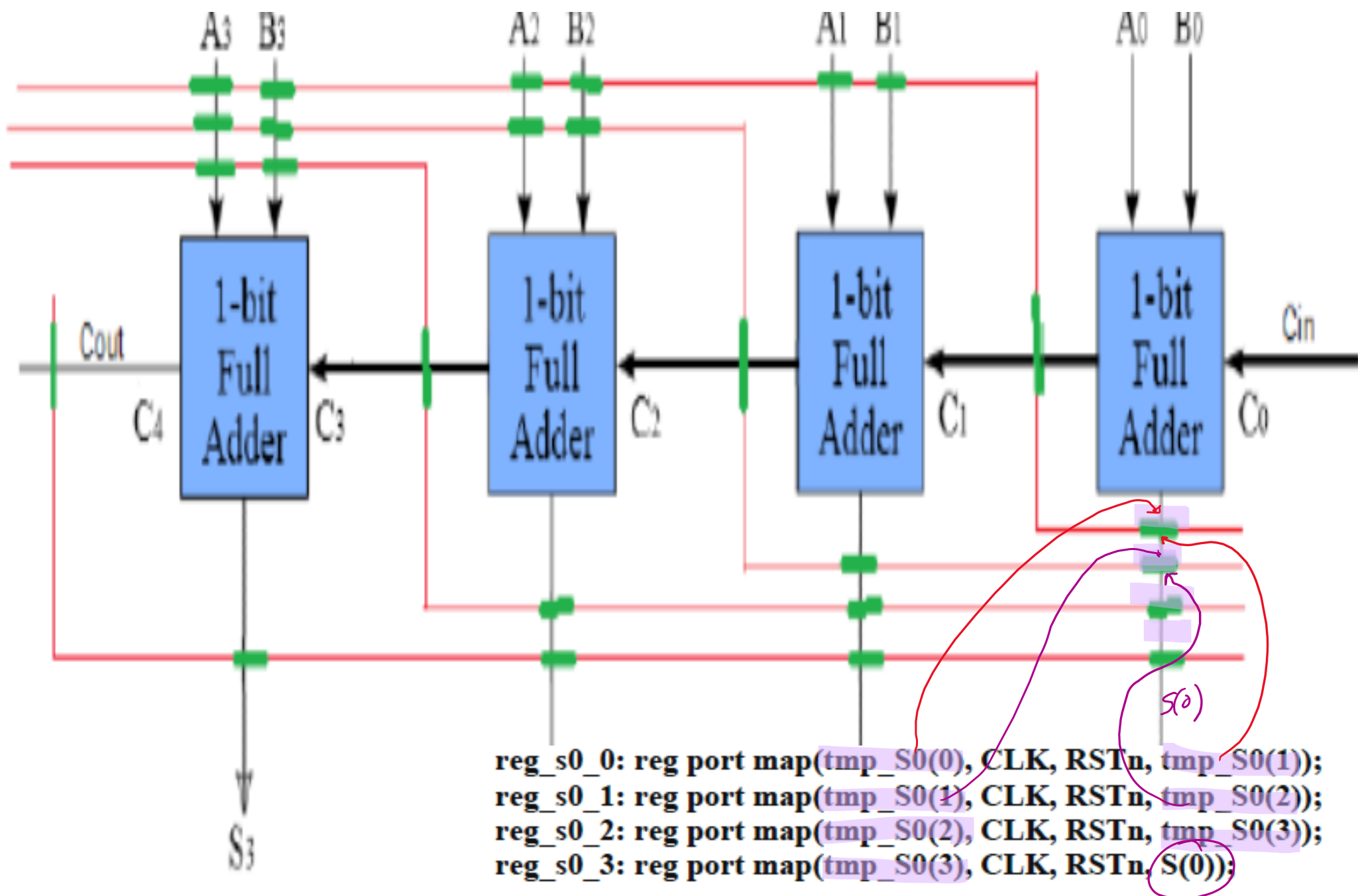
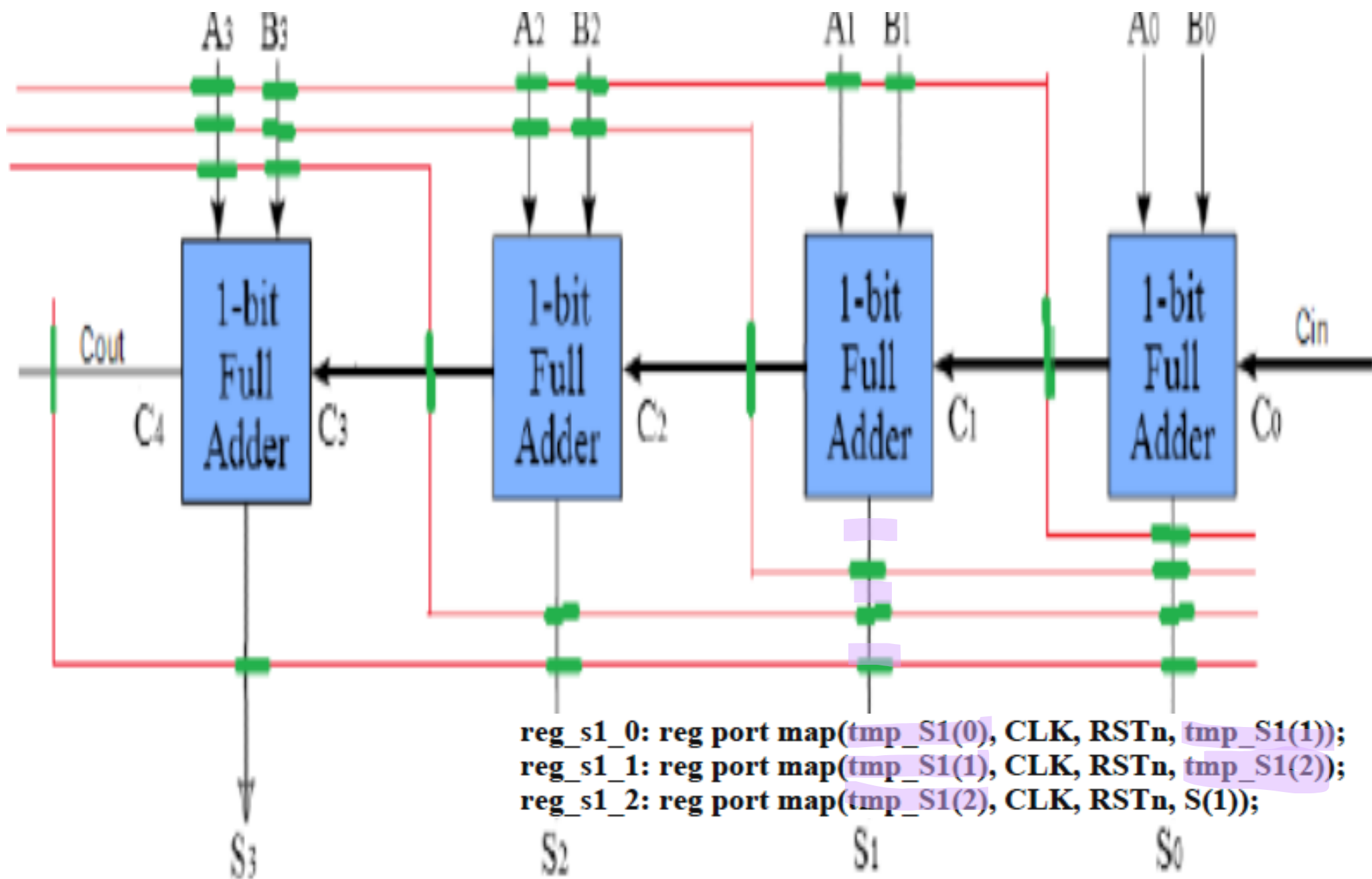
```
signal tmp_S0 : std_logic_vector(3 downto 0);
```



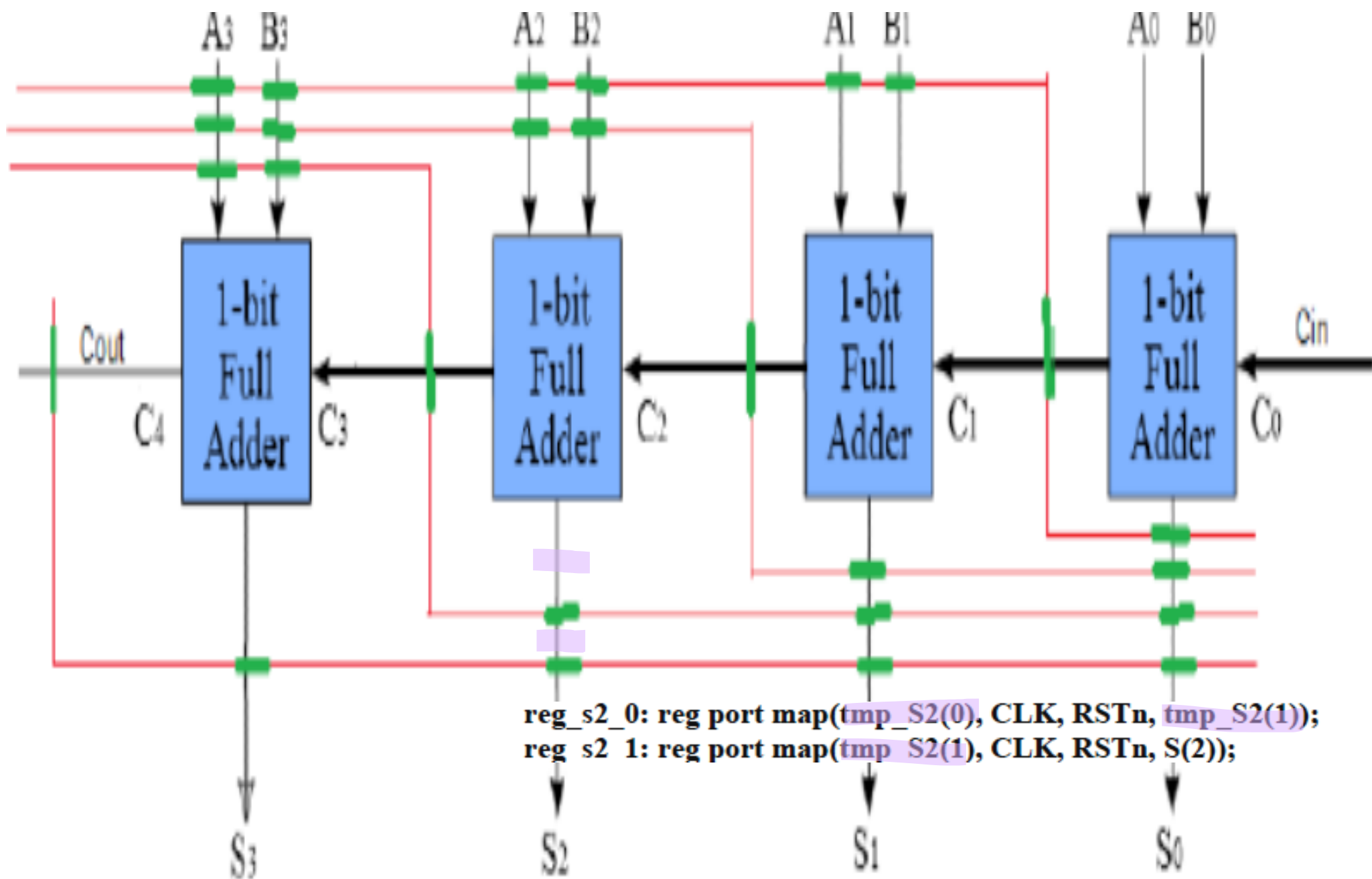
```
signal tmp_S1: std_logic_vector(2 downto 0);
```




```


signal tmp_S2 : std_logic_vector(1 downto 0);

```
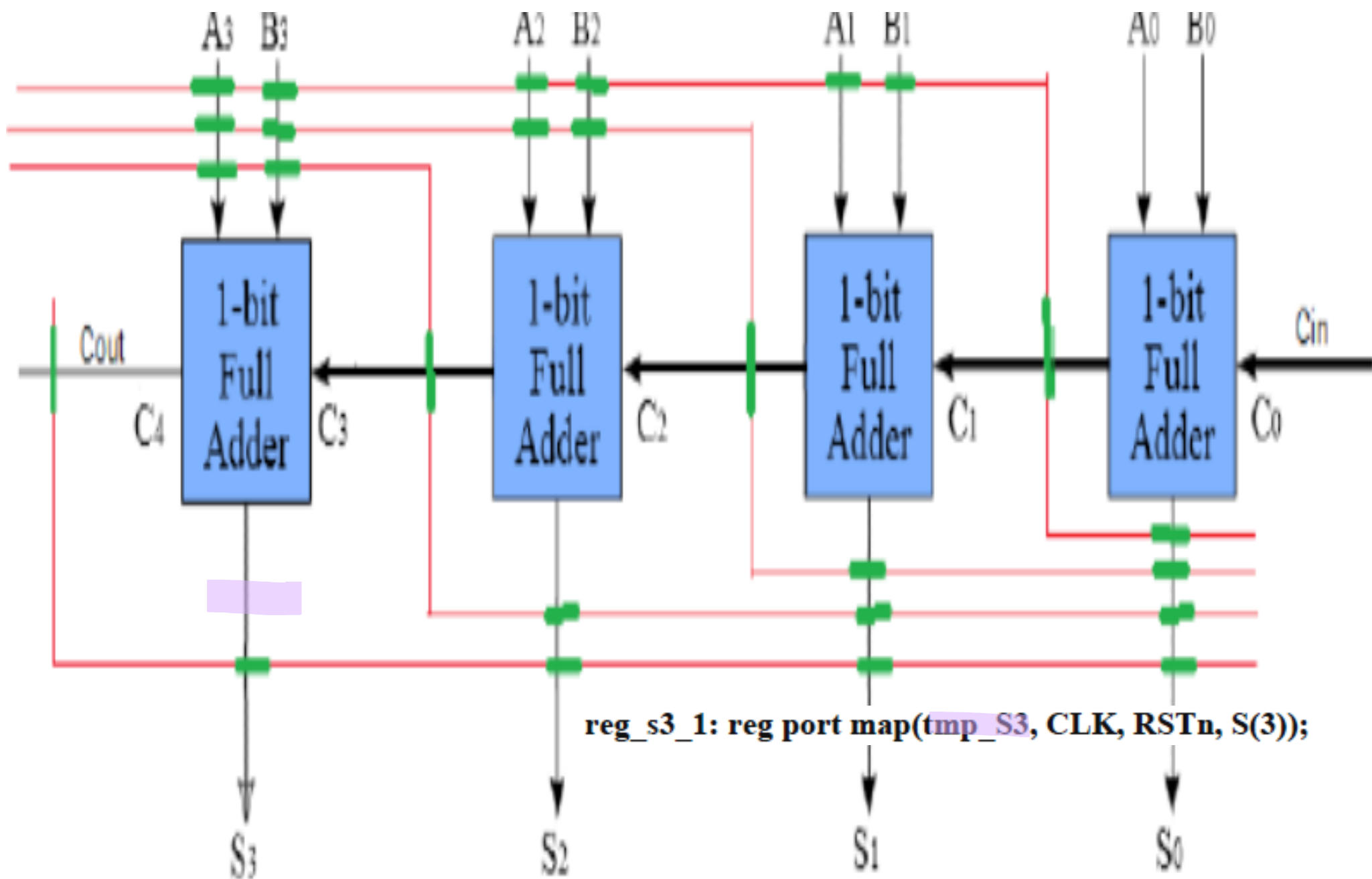
```
signal tmp_S3 : std_logic;
```




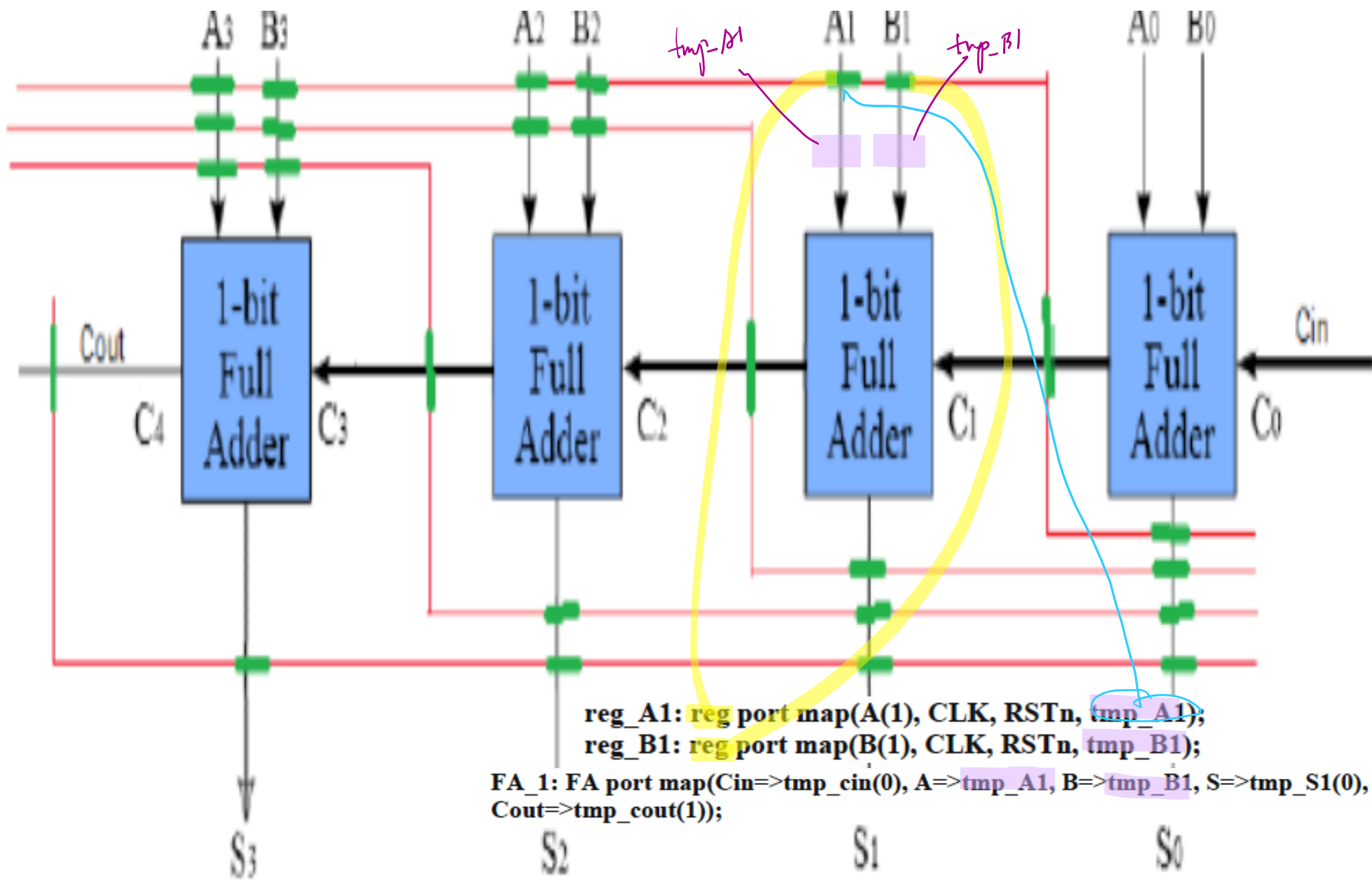
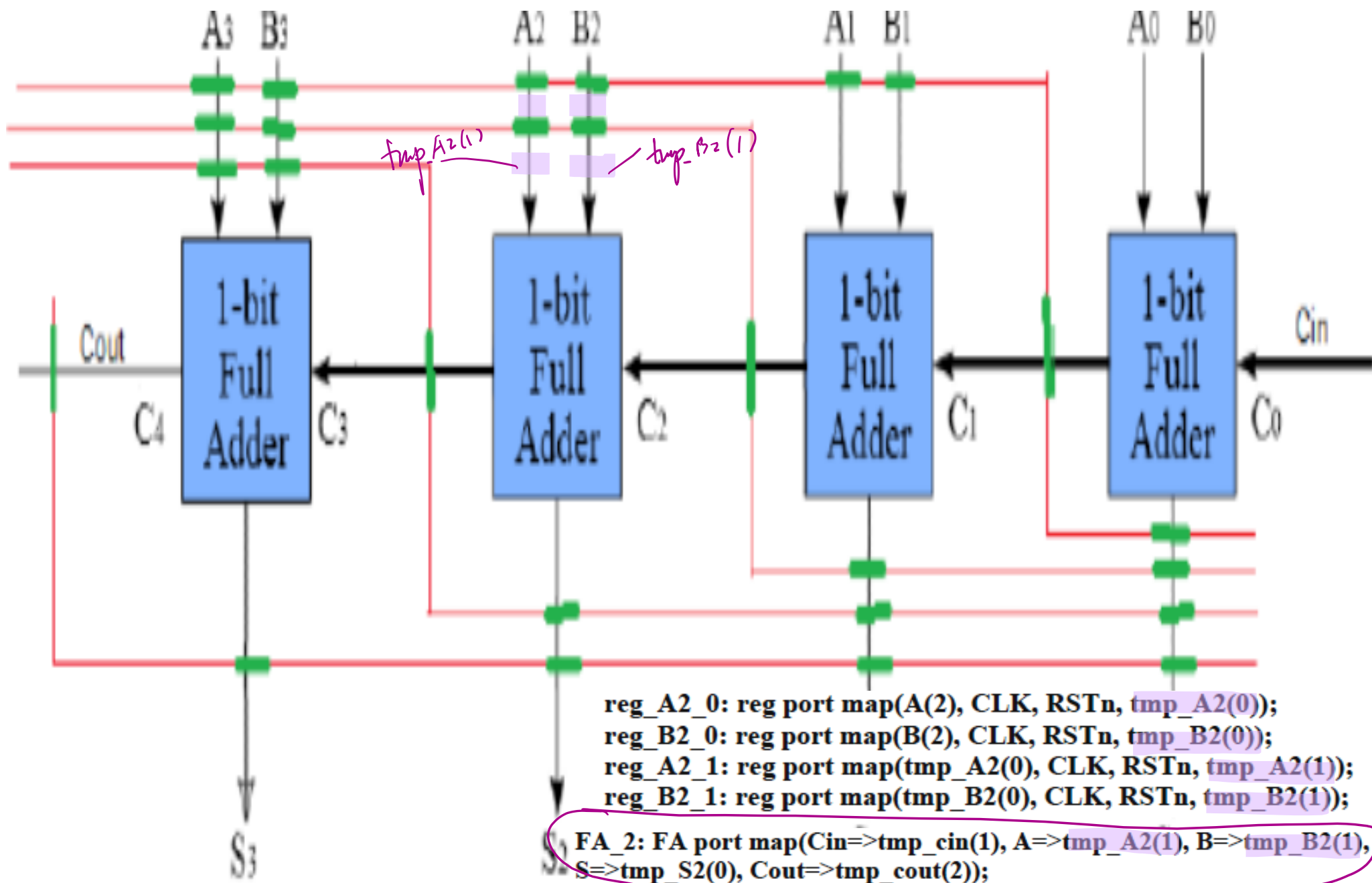
```

signal tmp_A2 : std_logic_vector(1 downto 0);
signal tmp_B2 : std_logic_vector(1 downto 0);


```

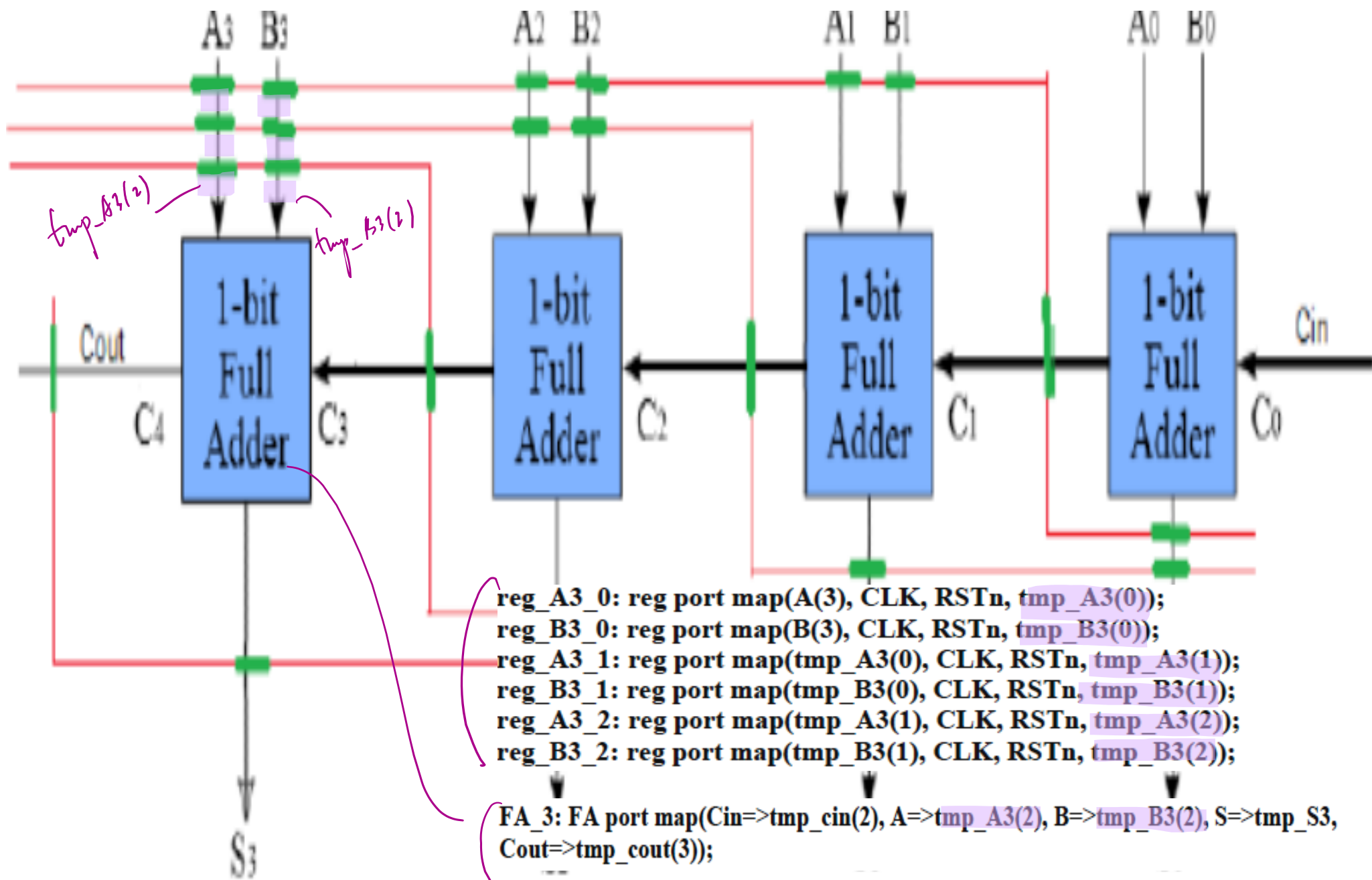

```

signal tmp_A3 : std_logic_vector(2 downto 0);
signal tmp_B3 : std_logic_vector(2 downto 0);

```

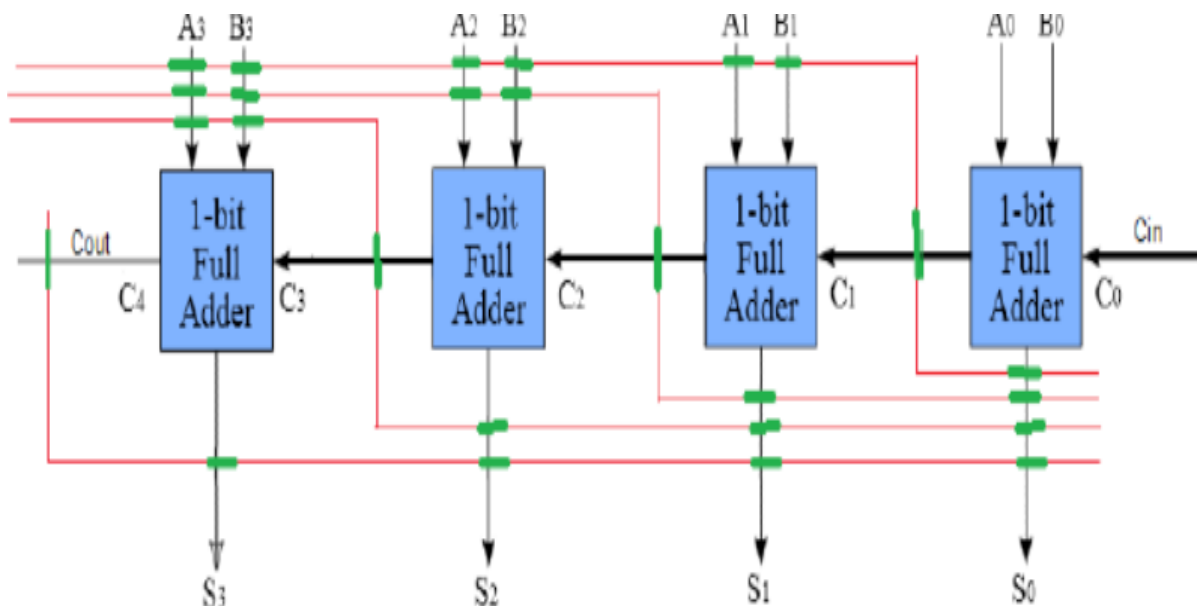

architecture behaviour of reg is
begin
process(CLK, RSTn)
begin
if RSTn = '0' then
Q <= '0';
elsif rising_edge(clk) then
Q <= D;
end if;
end process;
end architecture;

ARCHITECTURE behaviour OF FA is
begin
S <= A XOR B XOR Cin ;
Cout <= (A AND B) OR (Cin AND A) OR (Cin AND B) ;
end architecture;

```
reg_s0_0: reg port map(tmp_S0(0), CLK, RSTn, tmp_S0(1));
reg_s0_1: reg port map(tmp_S0(1), CLK, RSTn, tmp_S0(2));
reg_s0_2: reg port map(tmp_S0(2), CLK, RSTn, tmp_S0(3));
reg_s0_3: reg port map(tmp_S0(3), CLK, RSTn, S(0));
reg_s1_0: reg port map(tmp_S1(0), CLK, RSTn, tmp_S1(1));
reg_s1_1: reg port map(tmp_S1(1), CLK, RSTn, tmp_S1(2));
reg_s1_2: reg port map(tmp_S1(2), CLK, RSTn, S(1));
reg_s2_0: reg port map(tmp_S2(0), CLK, RSTn, tmp_S2(1));
reg_s2_1: reg port map(tmp_S2(1), CLK, RSTn, S(2));
reg_s3_1: reg port map(tmp_S3, CLK, RSTn, S(3));
reg_cout0: reg port map(tmp_cout(0), CLK, RSTn, tmp_cin(0));
reg_cout1: reg port map(tmp_cout(1), CLK, RSTn, tmp_cin(1));
reg_cout2: reg port map(tmp_cout(2), CLK, RSTn, tmp_cin(2));
reg_cout3: reg port map(tmp_cout(3), CLK, RSTn, Cout);
reg_A1: reg port map(A(1), CLK, RSTn, tmp_A1);
reg_B1: reg port map(B(1), CLK, RSTn, tmp_B1);
reg_A2_0: reg port map(A(2), CLK, RSTn, tmp_A2(0));
reg_B2_0: reg port map(B(2), CLK, RSTn, tmp_B2(0));
reg_A2_1: reg port map(tmp_A2(0), CLK, RSTn, tmp_A2(1));
reg_B2_1: reg port map(tmp_B2(0), CLK, RSTn, tmp_B2(1));
reg_A3_0: reg port map(A(3), CLK, RSTn, tmp_A3(0));
reg_B3_0: reg port map(B(3), CLK, RSTn, tmp_B3(0));
reg_A3_1: reg port map(tmp_A3(0), CLK, RSTn, tmp_A3(1));
reg_B3_1: reg port map(tmp_B3(0), CLK, RSTn, tmp_B3(1));
reg_A3_2: reg port map(tmp_A3(1), CLK, RSTn, tmp_A3(2));
reg_B3_2: reg port map(tmp_B3(1), CLK, RSTn, tmp_B3(2));
```

-- Component declarations

```
component FA PORT (Cin, A, B: IN STD_LOGIC ; Cout, S: OUT STD_LOGIC ) ;
end component;
```

```
component reg port(D, CLK, RSTn: in std_logic; Q: out std_logic);
end component;
```

```
FA_0: FA port map(Cin=>Cin, A=>A(0), B=>B(0), S=>tmp_S0(0),
Cout=>tmp_cout(0));
FA_1: FA port map(Cin=>tmp_cin(0), A=>tmp_A1, B=>tmp_B1, S=>tmp_S1(0),
Cout=>tmp_cout(1));
FA_2: FA port map(Cin=>tmp_cin(1), A=>tmp_A2(1), B=>tmp_B2(1),
S=>tmp_S2(0), Cout=>tmp_cout(2));
FA_3: FA port map(Cin=>tmp_cin(2), A=>tmp_A3(2), B=>tmp_B3(2), S=>tmp_S3,
Cout=>tmp_cout(3));
```